

Combinational Circuits: Design

Digital Design and Computer Architecture

Mohammad Sadrosadati

Frank K. Gürkaynak

<http://safari.ethz.ch/ddca>

What will we learn

- **Converting desired functionality into Boolean equations**
- **Karnaugh Maps (simplification of equations)**
- **Circuits with more than one output**
- **Timing of combinational circuits**

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch (\overline{E})
 - If it is not open (\overline{O}) or
 - If they only serve cabbage (C)
- Write a truth table for determining if you will eat lunch (E):

<i>open</i> O	<i>only cabb.</i> C	<i>eat</i> E
0	0	
0	1	
1	0	
1	1	

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch (\overline{E})
 - If it is not open (\overline{O}) or
 - If they only serve cabbage (C)
- Write a truth table for determining if you will eat lunch (E)

<i>open</i>	<i>only cabb.</i>	<i>eat</i>
O	C	E
0	0	0
0	1	0
1	0	1
1	1	0

Some Definitions

- **Complement:** variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- **Implicant:** product (AND) of literals
 $(A \cdot B \cdot \bar{C}), (\bar{A} \cdot C), (B \cdot \bar{C})$
- **Minterm:** product (AND) that includes all input variables
 $(A \cdot B \cdot \bar{C}), (\bar{A} \cdot \bar{B} \cdot C), (\bar{A} \cdot B \cdot \bar{C})$
- **Maxterm:** sum (OR) that includes all input variables
 $(A + \bar{B} + \bar{C}), (\bar{A} + B + \bar{C}), (A + B + \bar{C})$

Sum-of-Products (SOP) Form

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	0
1	1	1

$$Y = F(A, B) = ?$$

- All Boolean equations can be written in SOP form
 - Each row in a truth table has a minterm
 - A minterm is a product (AND) of literals
 - Each minterm is TRUE for that row (and only that row)
 - *blackboard*
- Formed by ORing the minterms for which the output is TRUE

Sum-of-Products (SOP) Form

A	B	Y	minterm
0	0	0	$\overline{A} \overline{B}$
0	1	1	$\overline{A} B$
1	0	0	$A \overline{B}$
1	1	1	$A B$

$$\begin{aligned} Y &= F(A, B) \\ &= (\overline{A} \cdot B) + (A \cdot B) \end{aligned}$$

- All Boolean equations can be written in SOP form
 - Each row in a truth table has a minterm
 - A minterm is a product (AND) of literals
 - Each minterm is TRUE for that row (and only that row)
 - *blackboard*
- Formed by ORing the minterms for which the output is TRUE

The Dual: Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
 - Each row in a truth table has a maxterm
 - A maxterm is a sum (OR) of literals
 - Each maxterm is FALSE for that row (and only that row)
- Formed by **ANDing** the **maxterms** for which the output is **FALSE**

<i>A</i>	<i>B</i>	<i>Y</i>	maxterm
0	0	0	$A + B$
0	1	1	$A + \overline{B}$
1	0	0	$\overline{A} + B$
1	1	1	$\overline{A} + \overline{B}$

$$Y = F(A, B) = (A + B) \cdot (\overline{A} + B)$$

SOP & POS Form

■ SOP: sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

SOP or POS?

■ POS: product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

SOP & POS Form

■ SOP: sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$E = O \cdot \overline{C}$$

SOP shorter if the output is TRUE in only a few cases

■ POS: product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$E = (O + C) \cdot (O + \overline{C}) \cdot (\overline{O} + \overline{C})$$

POS is shorter if the output is FALSE in only a few cases

Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically


A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Y C		AB			
		00	01	11	10
0		1	0	0	0
1		1	0	0	0

Y C		AB			
		00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

- *Blackboard*
- *Works well for up to four variables*

Karnaugh Map Rules

- **Special order for bit combinations: 00, 01, 11, 10** 
(only one bit changes from one to next)
- **Every 1 in a K-map must be circled at least once**
- **Each circle must span a power of 2 (i.e. 1, 2, 4) squares in each direction**
- **Each circle must be as large as possible**
- **A circle may wrap around the edges of the K-map**
- **A “don't care” (X) is circled only if it helps minimize the equation**

Karnaugh Map Example

- Blackboard

Karnaugh maps with Don't Cares

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

<i>Y</i>		<i>AB</i>			
<i>CD</i>		00	01	11	10
	00				
	01				
	11				
	10				

Karnaugh maps with Don't Cares

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

<i>Y</i> <i>CD</i> \ <i>AB</i>		00	01	11	10
		00	01	11	10
00		1	0	X	1
01		0	X	X	1
11		1	1	X	X
10		1	1	X	X

Karnaugh maps with Don't Cares

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

<i>Y</i> <i>CD</i> \ <i>AB</i>					
		00	01	11	10
00		1	0	X	1
01		0	X	X	1
11		1	1	X	X
10		1	1	X	X


$$Y = A + \overline{B}\overline{D} + C$$

Is this useful?

- In modern engineering practice, computer programs called *logic synthesizers* produce simplified circuits from a description of the logic function (later in chap 4)
- For large problems, logic synthesizers are much more efficient than humans. For small problems, a human with a bit of experience can find a good solution by inspection.
- *Yes:* you understand the basic concepts.

From Logic to Gates

 - SOP (sum-of-products) leads to two-level logic
- Example: $Y = (\bar{A} \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot \bar{C}) + (A \cdot \bar{B} \cdot C)$



Circuit Schematics

- **Inputs: left (or top) side of a schematic**
- **Outputs: right (or bottom) side of a schematic**
- **Circuits should flow from left to right**
- **Straight wires are better than wires with multiple corners**


Circuit Schematic (cont.)

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect
at a T junction



wires connect
at a dot

 


 wires crossing
without a dot do
not connect



Multiple Output Circuits: Priority Circuit

 
- Output is the most significant TRUE input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0				
0	0	0	1				
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

Multiple Output Circuits : Priority Circuit

 
- Output is the most significant TRUE input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

Priority Encoder Hardware *“by inspection”*

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

 

- We could write sum-of-products form and reduce the equations. From the functional description :

- Y_3 is TRUE whenever A_3 is asserted, so $Y_3 = A_3$.
- Y_2 is TRUE if A_2 is asserted and A_3 is not asserted, so $Y_2 = \bar{A}_3 A_2$

Compressing the Truth Table: Don't Cares

Truth Table

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

Compressed with don't cares

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0


Additional logic levels: X and Z

■ So far we used only 1s and 0s for our circuits.

- For some cases we need several more, slightly strange, signals
- These do not encode information, but represent different levels or cases where the output is neither 1 or 0


■ Contention: **X**

 - When a signal is being driven to 1 and 0 simultaneously
- Not a real level, could be any value (1, 0 or something in between)




■ High-impedance or tri-state: **Z**

 - When an output is not driving to any specific value
- Means the output is disconnected
- Not a real level, some other output is able to determine the level



Contention: X

 


■ Usually a problem

- Two outputs drive one node to opposite values
- Normally there should only be one driver for every connection.


■ Warning: “don’t care” and “contention” are both called X

- These are not the same
- Verilog (we will see later) uses X for both, VHDL uses ‘-’ for don’t care, and ‘X’ for contention
- Don’t care: degree of freedom that is fixed at implementation time
- Contention: a bug really, undetermined behaviour

Floating: Z

 

 
- Output is called: Floating, high impedance, tri-stated, high-Z
- Floating output might be 0, 1, or somewhere in between
- Example: tri-state buffer



E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

Tristate Busses

 - **Floating nodes are used in tri-state busses**
 - Many different drivers share one common connection
 - *Exactly one driver is active* at any time
 - All the other drivers are *“disconnected”*
 - The disconnected drivers are said to be *floating*, allowing exactly one node to drive.
 - More than one input can listen to the shared bus without problems




Combinational Building Blocks

- **Combinational logic is often grouped into larger building blocks to build more complex systems**
- **Hide the unnecessary gate-level details to emphasize the function of the building block**
- **We have already studied some building blocks**
 - full adders
 - priority circuits
- **We now look at:**
 - multiplexers
 - decoders

Multiplexer (Mux)

 
- Selects between one of N inputs to connect to the output.
- Needs $\log_2 N$ -bit control input
- 2:1 Mux Example:



S	D_1	D_0	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Multiplexer (Mux)

 
- Selects between one of N inputs to connect to the output.
- Needs $\log_2 N$ -bit control input
- 2:1 Mux Example:




S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0	<i>Compressed version</i>	
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

4:1 Multiplexer Implementations


using two-level logic

 

using tristate buffers

 


using tree of 2:1 muxes

 


Logic Using Multiplexers

- Implement $Y = AB$ using a multiplexer; use A as a control

Logic Using Multiplexers

 


(a)

 

(b)

Logic Using Multiplexers

 

- We start with an ordinary truth table, and then combine pairs of rows to eliminate the rightmost input variable by expressing the output in terms of this variable.

Logic using Multiplexers

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$


(a)

Logic using Multiplexers

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$

(a)

 


(b)

- In general, a 2^N -input multiplexer can be programmed to perform any N-input logic function by applying 0's and 1's to the appropriate data inputs: *it's a lookup table!*


Decoders

 - N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0	
0	0	0	0	0	1	← These are exactly the minterms
0	1	0	0	1	0	
1	0	0	1	0	0	
1	1	1	0	0	0	


Decoder Implementation

 

A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 


Logic using Decoders

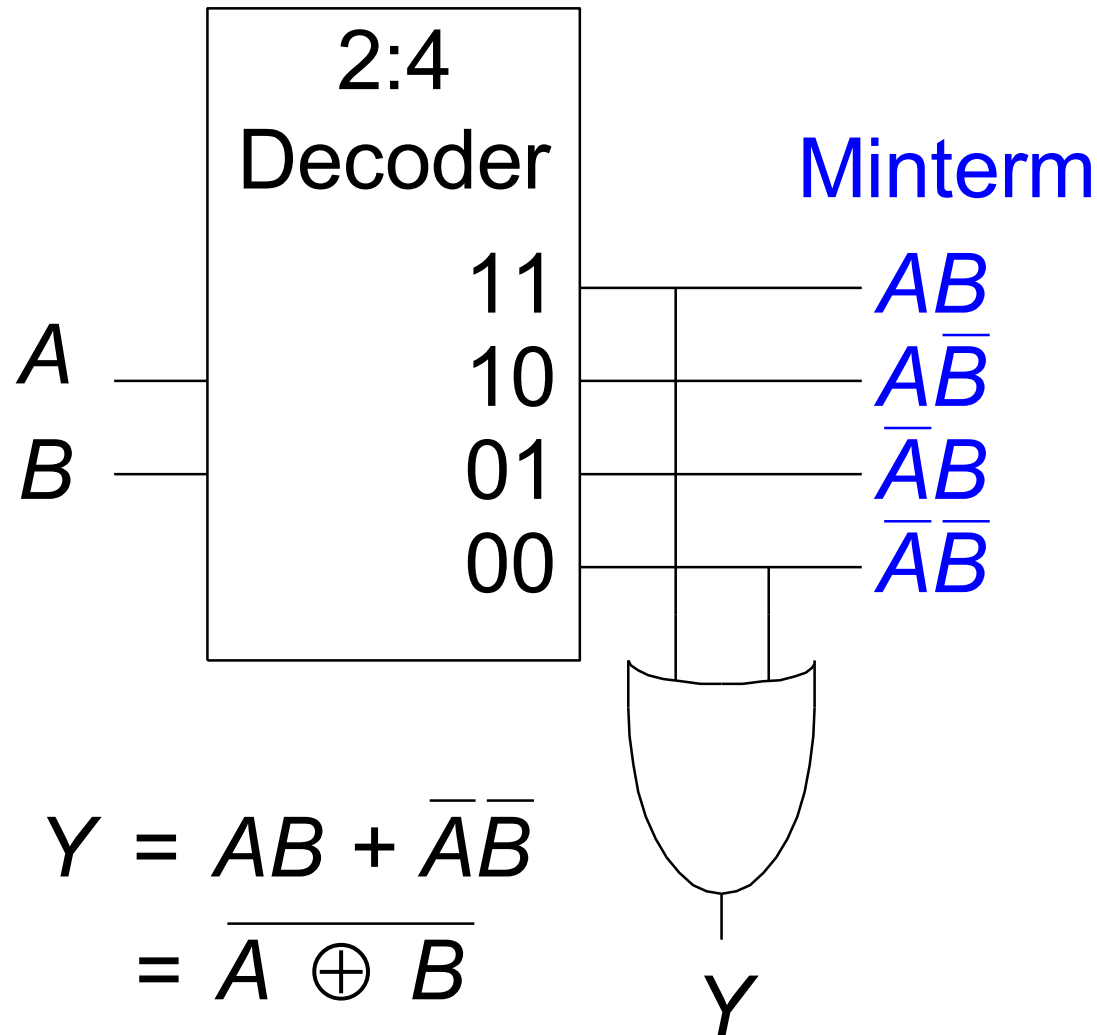


Timing

 - Until now, we investigated mainly functionality
- What determines how fast a circuit is and how can we make faster circuits?



Propagation and Contamination Delay

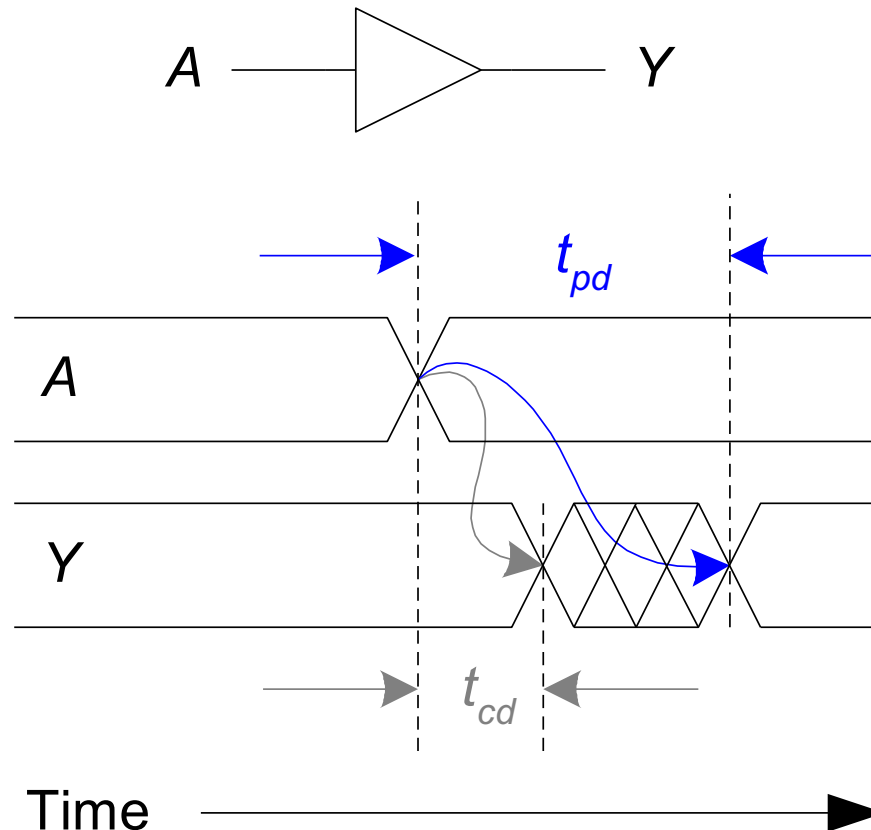- **Propagation delay:** t_{pd} = max delay from input to output
- **Contamination delay:** t_{cd} = min delay from input to output



Propagation & Contamination Delay


■ Delay is caused by

- Capacitance and resistance in a circuit
- Speed of light limitation (not as fast as you think!)

■ Reasons why t_{pd} and t_{cd} may be different:

- Different rising and falling delays
- Multiple inputs and outputs, some of which are faster than others
- Circuits slow down when hot and speed up when cold

Critical (Long) and Short Paths

 

- Critical (Long) Path:

$$t_{pd} = 2 t_{pd_AND} + t_{pd_OR}$$

- Short Path:


$$t_{cd} = t_{cd_AND}$$

Propagation times


Table 2.7 Timing specifications for multiplexer circuit elements

Gate	t_{pd} (ps)
NOT	30
2-input AND	60
3-input AND	80
4-input OR	90
tristate (A to Y)	50
tristate (enable to Y)	35

Propagation times

 
 
$$\begin{aligned}
 t_{pd_sy} &= t_{pd_INV} + t_{pd_AND3} + t_{pd_OR4} \\
 &= 30 \text{ ps} + 80 \text{ ps} + 90 \text{ ps} \\
 &= 200 \text{ ps} \\
 \text{(a)} \quad t_{pd_dy} &= t_{pd_AND3} + t_{pd_OR4} \\
 &= 170 \text{ ps}
 \end{aligned}$$



$$\begin{aligned}
 t_{pd_sy} &= t_{pd_INV} + t_{pd_AND2} + t_{pd_TRI_SY} \\
 &= 30 \text{ ps} + 60 \text{ ps} + 35 \text{ ps} \\
 &= 125 \text{ ps} \\
 \text{(b)} \quad t_{pd_dy} &= t_{pd_TRI_AY} \\
 &= 50 \text{ ps}
 \end{aligned}$$


Figure 2.73 4:1 multiplexer propagation delays:
(a) two-level logic,
(b) tristate

Glitches

- **Glitch: when a single input change causes multiple output changes**
- **Glitches don't cause problems because of synchronous design conventions (which we'll talk about in a bit)**
- **But it's important to recognize a glitch when you see one in timing diagrams**

Glitch Example


 
- What happens when $A = 0$, $C = 1$, B falls (1→0) ?




		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$

Glitch Example (cont.)

 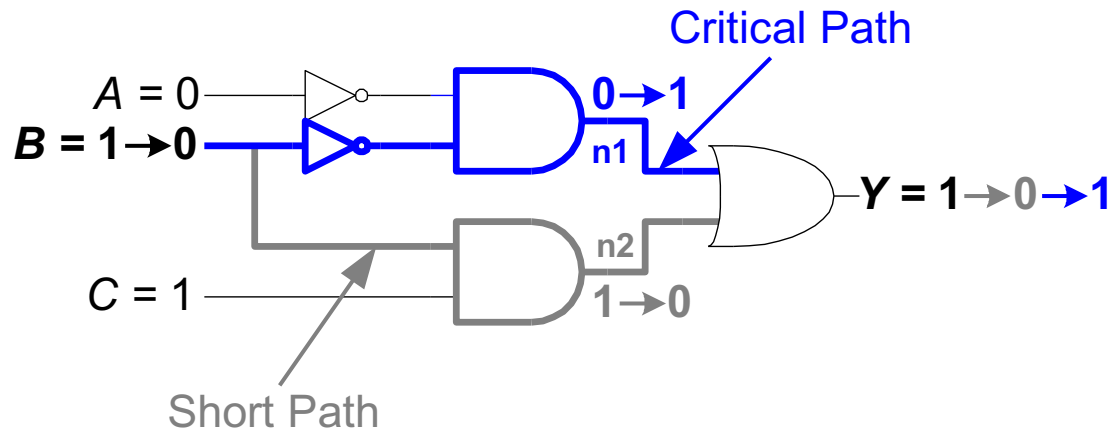

Noticing a Glitch


 


		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \overline{A}\overline{B} + BC$$

- In general, a glitch can occur when a change in a single variable crosses the boundary between two prime implicants in a K-map.
- Transition on B (ABC=001 to ABC 011) moves from one prime implicant to the other.
- We can eliminate the glitch by adding redundant implicants to the K-map to cover these boundaries.

Fixing the Glitch

  

Why Understand Glitches?

- Glitches don't cause problems because of synchronous design conventions (which we'll talk about later)
- But it's important to recognize a glitch when you see one in simulations or on an oscilloscope
- Can't get rid of all glitches – simultaneous transitions on multiple inputs can also cause glitches

What have we learned?

- **How to construct truth tables**
- **Converting truth tables into SOP and POS form**
- **Using Karnaugh maps to simplify Boolean Equations**
- **Timing of combinational circuits**
 - Propagation delay: longest time through the circuit
 - Contamination delay: shortest time in which the output reacts