

Sequential Logic Design

Digital Design and Computer Architecture

Mohammad Sadrosadati

Frank K. Gürkaynak

<http://safari.ethz.ch/ddca>

What will we learn?

- **Combinational and Sequential Circuits**
- **How can a circuit remember a value**
- **Different types of memorizing elements**
- **Finite State Machines**

Introduction

- Outputs of combinational circuit depend **ONLY** on current input values.
- Outputs of sequential logic depend on current *and* prior input values – it has **memory**.
- **Some definitions:**
 - ***State***: all the information about a circuit necessary to explain its future behavior
 - ***Latches and flip-flops***: state elements that store one bit of state
 - ***Synchronous sequential circuits***: combinational logic followed by a bank of flip-flops

Sequential == Combinational + State

- **Largest part of a sequential circuit is combinational**
 - The only additional thing we need to learn is to store the **state**
 - Defining flip-flops (latches), registers should do the trick
- **Sequential circuits divide the operation into time slots**
 - At every time slot inputs (if there are any) are taken
 - **Present state** and inputs are used to calculate the **next state**
 - The **next state** is saved in the flip-flops (registers)
- **How fast we can finish the operation?**
 - The clock signal is used to move from one **state** to the **next state**
 - I.e. a 2 GHz clock has time steps of 500ps.
 - The work within a time slot is done by a **combinational** circuit.

Datapath vs Finite State Machine

RTL design


- **RTL is a generic way of defining digital circuits**
 - State is stored in registers
 - Every time slot, inputs and present state calculates the next state
 - Next state is stored in a register.
 - The clock moves the circuit from the present state to next state
- **RTL defines datapath circuits ...**
 - They process data and do the main work
- **... and Finite State machines**
 - Generate control signals for the datapath
- **The distinction makes life easier**

State Elements

- The state of a circuit influences its future behavior
- State elements store state
- Bistable circuits
 - SR Latch
 - D Latch
 - D Flip-flop

How can a circuit remember?

 
- **Bistable circuits can have two distinct states**
 - Once they are in one state, they will remain there.



- **The Loop keeps the state stable**

How can a circuit remember?

 
- Bistable circuits can have two distinct states
 - Once they are in one state, they will remain there.



- The Loop keeps the state stable

How can a circuit remember?

 - **Bistable circuits can have two distinct states**
 - Once they are in one state, they will remain there.




- **But how can we move from one state to another?**

How can a circuit remember?

- **Bistable circuits can have two distinct states**

 - Once they are in one state, they will remain there.




- **But how can we move from one state to another?**

- We add one switch to break the loop and at the same time add another switch that connects an input to the circuit


The D Latch

 - D Latch is the basic bi-stable circuit used in modern CMOS.
 - The clock controls the switches. **Only one is active** at a time.
 - Traditionally the input is called D (Data) and the output Q




The D Latch has two modes

 - Latch mode, loop is active, input disconnected, keeps state




The D Latch has two modes

 - Latch mode, loop is active, input disconnected, keeps state



 - Transparent mode, loop is inactive, input is connected and propagates to output



Summary D Latch

- **Simple bi-stable circuit**

- Can be used to store a 0 or a 1.

- **Has two modes**

- *Transparent mode*: input propagates to output
 - *Latch mode*: the output is stored (also called *opaque mode*)

- **The clock controls the modes of operation.**


- Depending on the type, it might be latch is transparent when $\text{Clk}=1$ or latch is transparent when $\text{Clk}=0$

Rising edge triggered D Flip-Flop

- Two inputs: CLK, D

- **Function**

 - The flip-flop “samples” D on the rising edge of CLK
 - When CLK rises from 0 to 1, D passes through to Q
 - Otherwise, Q holds its previous value
 - Q changes only on the rising edge of CLK
- **A flip-flop is called an edge-triggered device because it is activated on the clock edge**



D Flip-Flop Internal Circuit


- Two back-to-back latches (L1 and L2) controlled by complementary clocks

- *When CLK = 0*

- L1 is transparent
- L2 is opaque
- D passes through to N1



- *When CLK = 1*

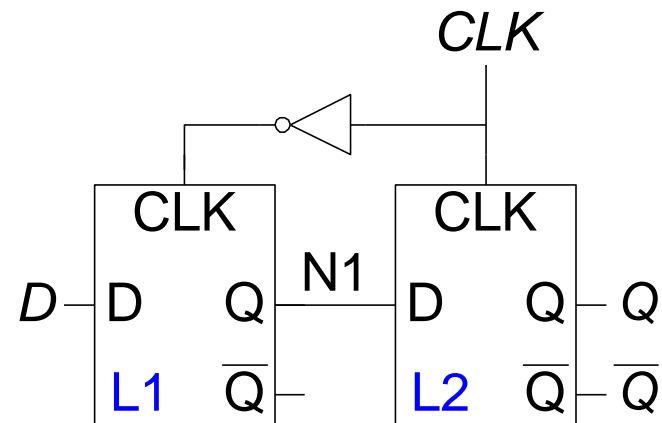- L2 is transparent
- L1 is opaque
- N1 passes through to Q






- Thus, on the edge of the clock (when CLK rises from 0 to 1)
- D passes through to Q

D Flip-Flop vs. D Latch

 
 


D Flip-Flop vs. D Latch

   

Registers

  - Multiple parallel flip-flops that store more than 1 bit




Enabled Flip-Flops

■ Inputs: CLK, D, EN

- The enable input (EN) controls when new data (D) is stored

■ Function

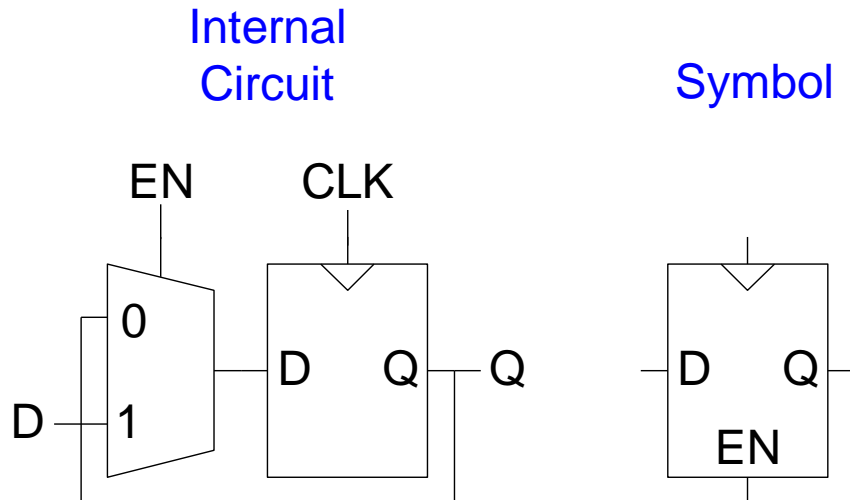- **EN = 1**: D passes through to Q on the clock edge
- **EN = 0**: the flip-flop retains its previous state



Resettable Flip-Flops



■ Inputs: CLK, D, Reset

- The Reset is used to set the output to 0.

■ Function:

- *Reset = 1:* Q is forced to 0
- *Reset = 0:* the flip-flop behaves like an ordinary D flip-flop

Symbols

  

Resettable Flip-Flops

- **Two types:**
 - Synchronous: resets at the clock edge only
 - Asynchronous: resets immediately when $\text{Reset} = 1$
- **Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop (see Exercise 3.10)**
- **Synchronously resettable flip-flop?**


Resettable Flip-Flops

- **Two types:**

- Synchronous: resets at the clock edge only
- Asynchronous: resets immediately when Reset = 1

- **Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop (see Exercise 3.10)**

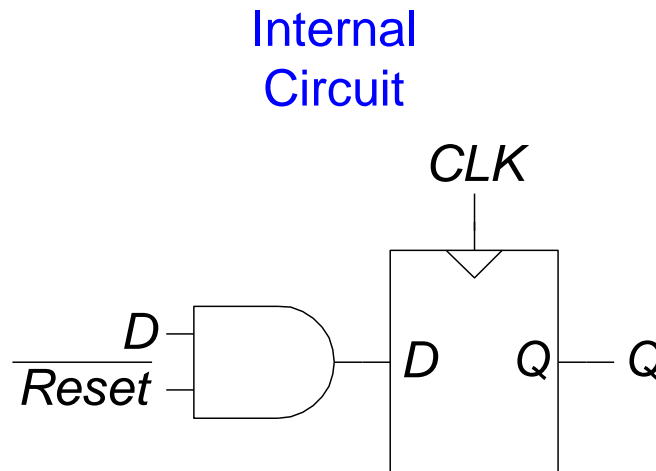
- **Synchronously resettable flip-flop?**



Settable Flip-Flops

- Inputs: CLK, D, Set
- Function:
 - **Set = 1**: Q is set to 1
 - **Set = 0**: the flip-flop behaves like an ordinary D flip-flop


Symbols

 

Finite State Machine (FSM) consists of:


■ State register:

 - Store the current state and
- Load the next state at the clock edge
- Sequential circuit




■ Next state logic

 - Determines what the next state will be
- Combinational circuit



■ Output logic

 - Generates the outputs
- Combinational Circuit




Finite State Machine (FSM)

- **FSMs get their name because a circuit with k registers can be in one of a finite number (2^k) of unique states.**


Finite State Machines (FSMs)

- Next state is determined by the current state and the inputs
- Two types of finite state machines differ in the output logic:
 - **Moore FSM**: outputs depend only on the current state
 - **Mealy FSM**: outputs depend on the current state and the inputs

Moore FSM

 


Mealy FSM

 

Finite State Machine Example

■ Traffic light controller

 
- **2 inputs:** Traffic sensors: T_A , T_B (TRUE when there's traffic)
- **2 outputs:** Lights: L_A , L_B



FSM Black Box

■ Inputs: CLK, Reset, T_A , T_B


■ Outputs: L_A , L_B

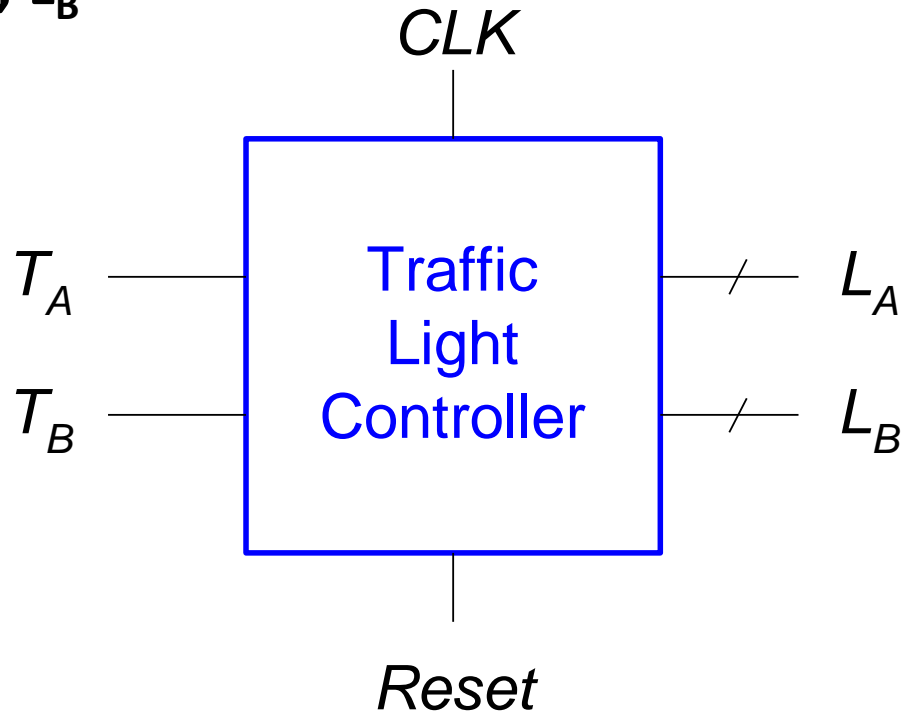

FSM State Transition Diagram

- **Moore FSM: outputs labeled in each state**



- States: Circles
- Transitions: Arcs

 

FSM State Transition Diagram

■ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

  

FSM State Transition Table

Current State	Inputs		Next State
S	T _A	T _B	S'
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

FSM State Transition Table

Current State	Inputs		Next State
S	T _A	T _B	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X		
0	0	1	X		
0	1	X	X		
1	0	X	0		
1	0	X	1		
1	1	X	X		

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

FSM Encoded State Transition Table

Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S'_1	S'_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \text{ xor } S_0$$

Simplification (Inspection or K-Maps)

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

FSM Output Table

Current State		Outputs	
S_1	S_0	L_A	L_B
0	0		
0	1		
1	0		
1	1		

FSM Output Table

Current State		Outputs	
S_1	S_0	L_A	L_B
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow

Output	Encoding
green	00
yellow	01
red	10

FSM Output Table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

FSM Output Table

Current State		Outputs			
S_1	S_0	L_{A1}	L_{A0}	L_{B1}	L_{B0}
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10



$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} \cdot S_0$$

$$L_{B1} = \overline{S_1}$$



$$L_{B0} = S_1 \cdot S_0$$

FSM Schematic: State Register

  



(a)

FSM Schematic: Next State Logic

 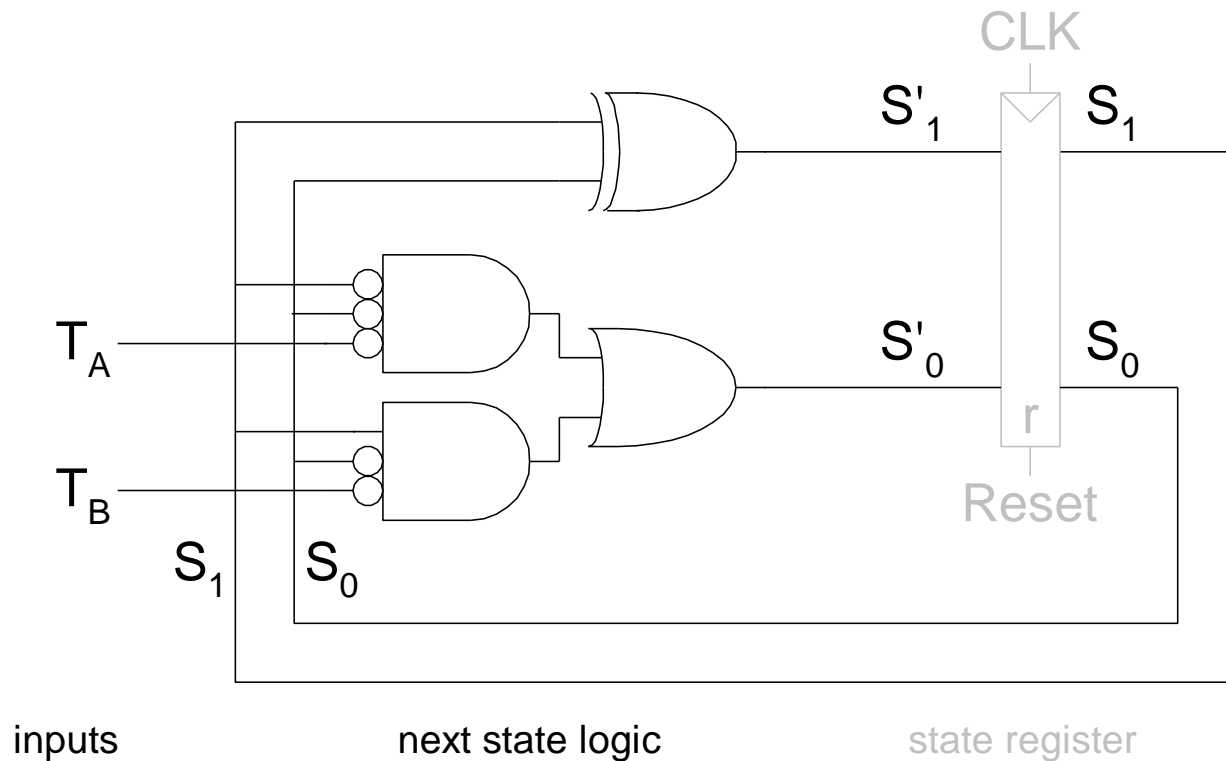



(a)

FSM Schematic: Output Logic

 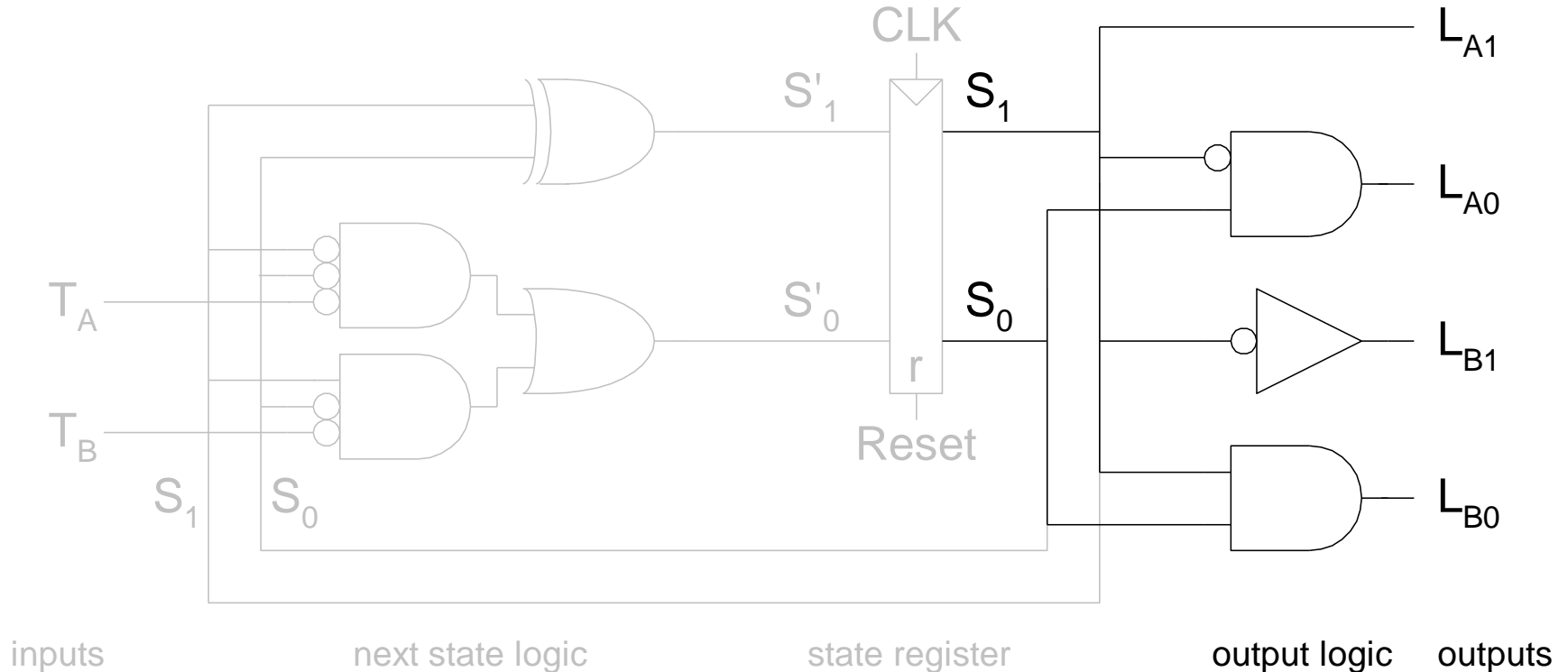

(a)

FSM Timing Diagram

  


FSM State Encoding

- **Binary encoding: i.e., for four states, 00, 01, 10, 11**
- **One-hot encoding**
 - One state bit per state
 - Only one state bit is HIGH at once
 - I.e., for four states, 0001, 0010, 0100, 1000
 - Requires more flip-flops
 - Often next state and output logic is simpler


Moore vs. Mealy FSM

- **Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last four digits it has crawled over are 1101. Design Moore and Mealy FSMs of the snail's brain.**

Moore FSM

 


Mealy FSM

 


State Transition Diagrams (snail - 1101)

Moore FSM

 

- Mealy FSM: arcs indicate input/output

Mealy FSM

 

Moore FSM State Transition Table

Current State			Inputs	Next State		
S_2	S_1	S_0	A	S'_2	S'_1	S'_0
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

Moore FSM State Transition Table

Current State			Inputs	Next State		
S_2	S_1	S_0	A	S'_2	S'_1	S'_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	0	1	0	1	0

State	Encoding
S0	000
S1	001
S2	010
S3	011
S4	100

Moore FSM Output Table

Current State			Output
S_2	S_1	S_0	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	

Moore FSM Output Table

Current State			Output
S_2	S_1	S_0	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1

$$Y = S_2$$

Mealy FSM State Transition and Output

Current State		Input	Next State		Output
S_1	S_0	A	S'_1	S'_0	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			


State	Encoding
S0	00
S1	01
S2	10
S3	11

Mealy FSM State Transition and Output


Current State		Input	Next State		Output
S_1	S_0	A	S'_1	S'_0	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	0
1	1	1	0	1	1

State	Encoding
S0	00
S1	01
S2	10
S3	11


Moore FSM Schematic

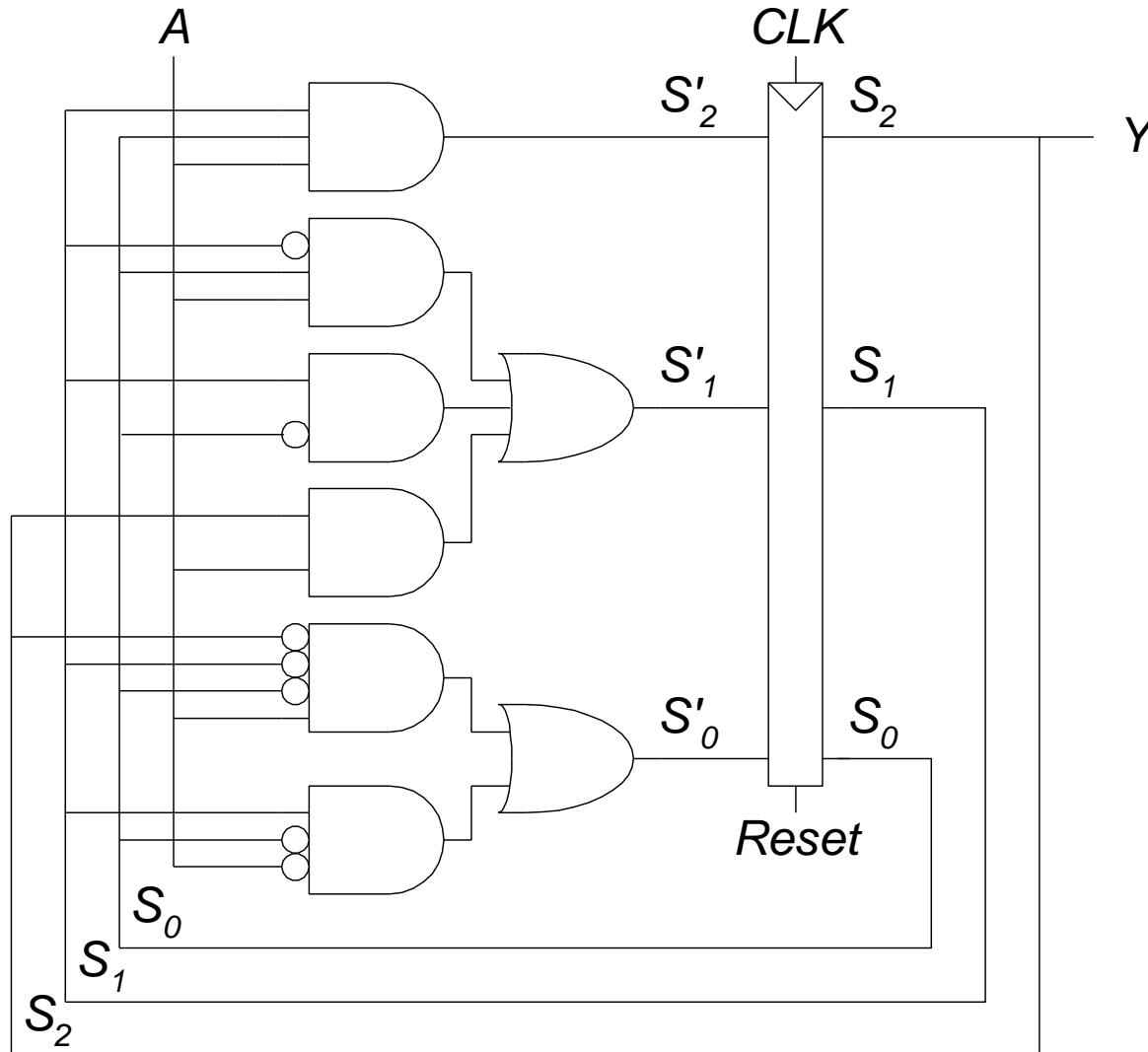

Mealy FSM Schematic

 


Moore and Mealy Timing Diagram

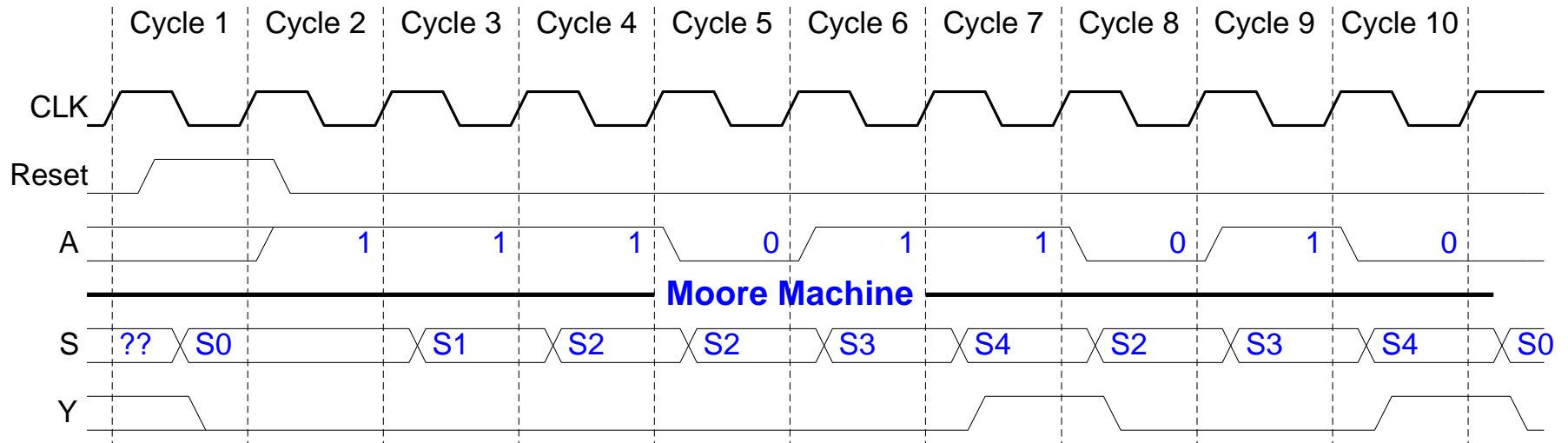

Why do we care if FSM is Moore/Mealy?

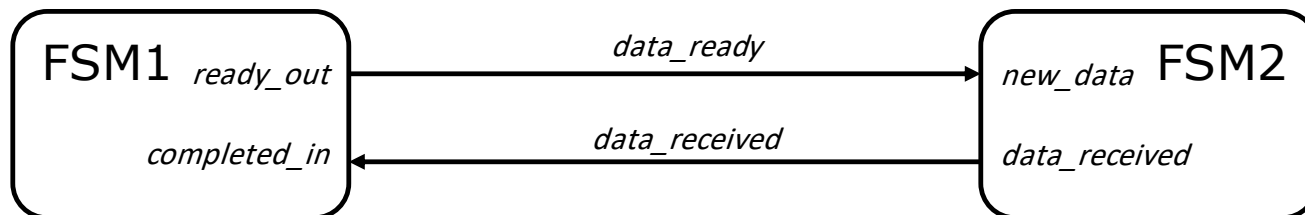- Is it to ask questions in an exam?
 - Traditionally, Frank always asks a Mealy/Moore question
- Remember combinational circuits
 - You are not supposed to have loops
- If two FSMs are connected, there will be **NO** loop if
 - At least one of them is MOORE
- There **CAN BE** a combinational loop if
 - Both FSMs are MEALY type.



Factoring State Machines


- Break complex FSMs into smaller interacting FSMs
- Example: Modify the traffic light controller to have a Parade Mode.
 - The FSM receives two more inputs: P , R
 - When $P = 1$, it enters Parade Mode and the Bravado Blvd. light stays green.
 - When $R = 1$, it leaves Parade Mode
- Designing complex FSMs is often easier if they can be broken down into multiple interacting simpler state machines such that the output of some machines is the input of others. This application of hierarchy and modularity is called **factoring of state machines**.

Parade FSM


Unfactored FSM





Factored FSM

 

Unfactored FSM State Transition Diagram

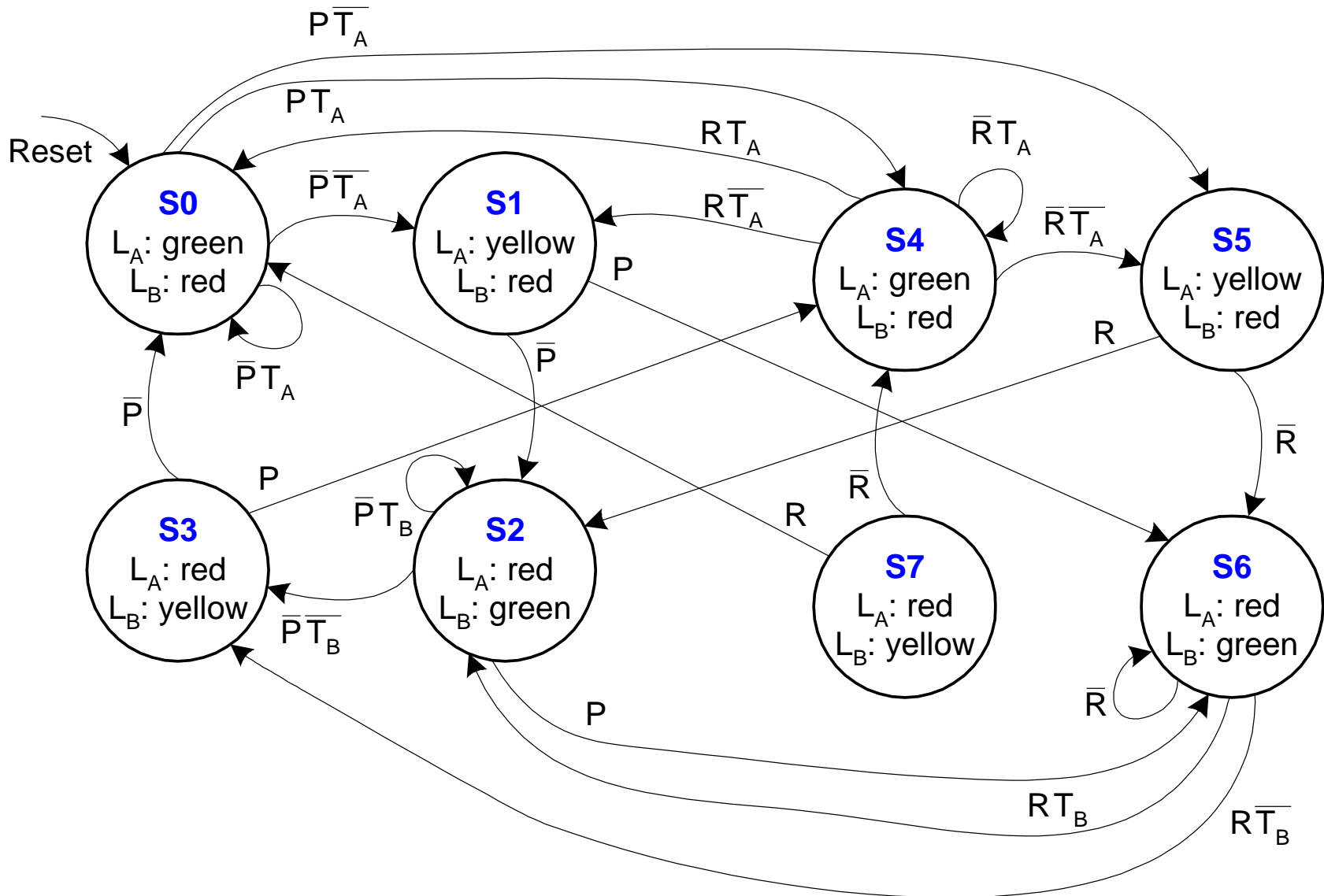

Factored FSM State Transition Diagram

 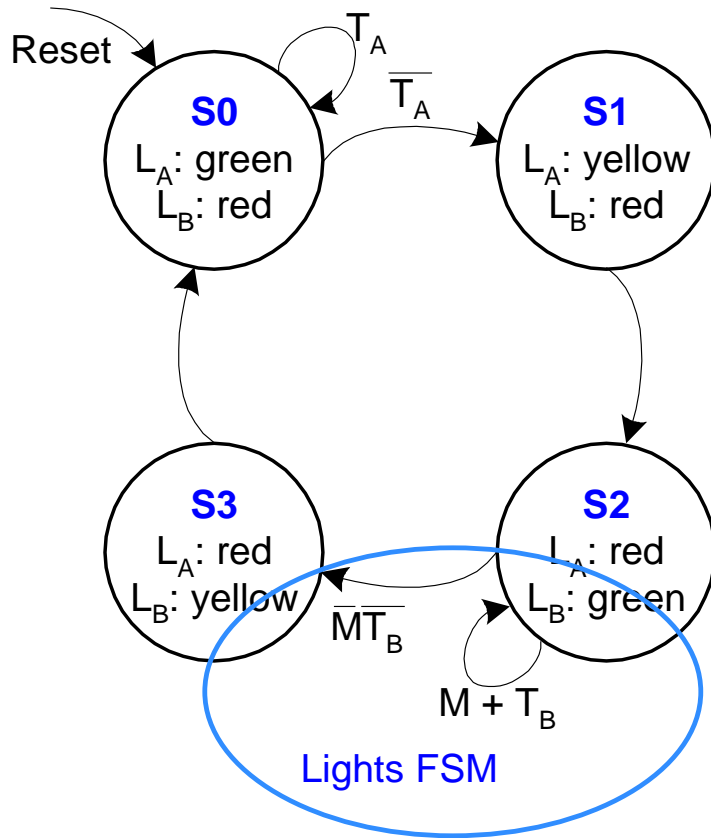

FSM Design Procedure

- **Prepare**
 - Identify the inputs and outputs
 - Sketch a state transition diagram
 - Write a state transition table
 - Select state encodings
- **For a *Moore* machine:**
 - Rewrite the state transition table with the selected state encodings
 - Write the output table
- **For a *Mealy* machine:**
 - Rewrite the combined state transition **and output table** with the selected state encodings
- **Write Boolean equations for the next state and output logic**
- **Sketch the circuit schematic**

What Did We Learn?

- **D Latch is the basic memorizing element**
 - Transparent mode, copies input to output
 - Latch mode, keeps content
- **(Rising) Edge Triggered Flip-Flops are more practical**
 - Input is copied to output when the clock rises from 0 to 1
- **Finite State Machines**
 - *Moore*, output depends on **only** the **current state**
 - *Mealy*, output depends on **current state and the inputs**.
- **Three Aspects of an FSM**
 - Holds the present state
 - Calculate the next state
 - Determine the outputs