

Digital Design & Computer Arch.

Lab 4 Supplement: Finite-State Machines

(Presentation by Aaron Zeller)

Frank K. Gürkaynak

Seyyedmohammad Sadrosadati

ETH Zurich

Spring 2024


[09. April 2024]

What Will We Learn?

- In Lab 4, you will **implement a finite-state machine using Verilog.**
- Design and implement a simple circuit that emulates the blinking lights of a Ford Thunderbird.
- Understand how the **clock signal is derived in the FPGA board.**
- **Write an FSM** that implements the Ford Thunderbird blinking sequence.

Tail Lights of a 1965 Ford Thunderbird

 - In this lab, you will design a finite-state machine to control the tail lights of a 1965 Ford Thunderbird.




Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Tail Lights of a 1965 Ford Thunderbird

- There are three lights on each side that operate in sequence to indicate the direction of a turn.

 Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e




Copyright from ClassicLEDs.com



Recall: Finite State Machines (FSMs)

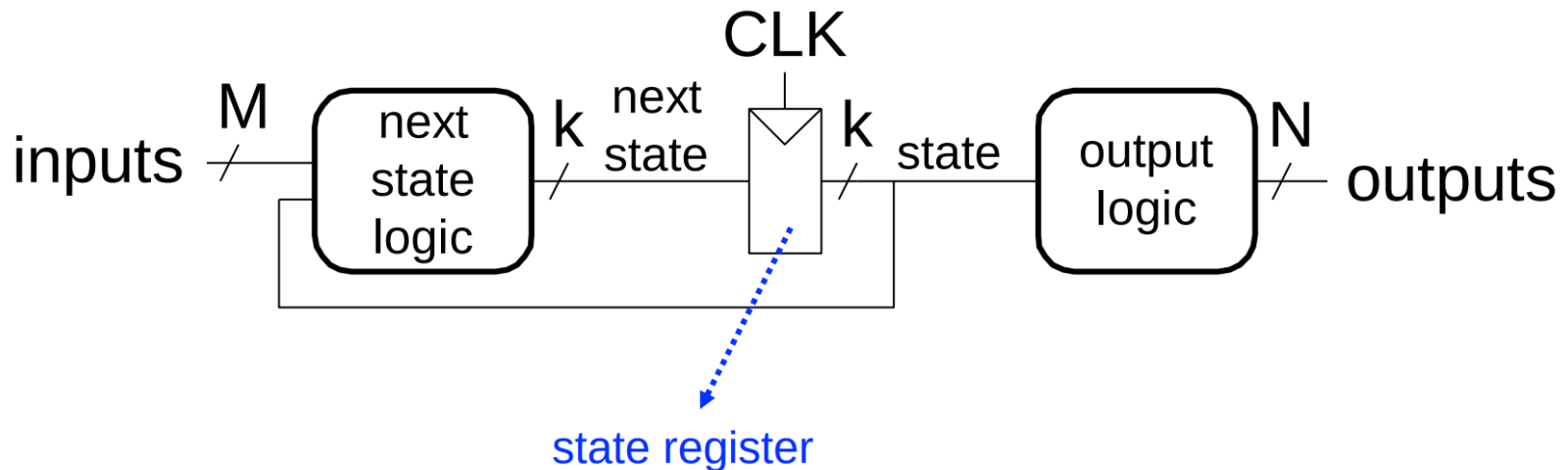- Each FSM consists of three parts:
 - next state logic
 - state register
 - output logic



At the beginning of the clock cycle, next state is latched into the state register

Part 1: FSM Design

- An FSM must do three things:
 - **Next State Logic:** Determine the next state from the present state and the inputs.
 - **Output Logic:** Determine the output signals based on the present state and input signals.
 - **State Register:** keeps track of the present state; must be updated at every clock cycle.

The manual contains the details of this FSM specifications.

Part 1: FSM Design

- An FSM must do three things:
 - **Next State Logic:** Determine the next state from the present state and the inputs.
 - **Output Logic:** Determine the output signals based on the present state and input signals.
 - **State Register:** keeps track of the present state; must be updated at every clock cycle.

For more details, please refer to [Lecture 7](#):

- Slides 26+: Finite State Machines
- Slides 28+: Moore vs. Mealy FSMs

Part 2: Verilog Implementation

- always blocks are used in **sequential circuits** and are used to create circuits involving flipflops.

Sensitivity List: Whenever a signal in the list changes the body of the always block is executed.



```
always @ (posedge clk, ...)  
    a <= b;  
    ...
```


Part 2: Verilog Implementation

- Do **not mix** assign statements and always blocks.
- **assign** is used to connect **wires**.
- **<=** and **=** inside **always blocks** are meant to set **registers** to some value.
 - **=** (blocking) : assignments are executed in sequential order.
 - **<=** (non-blocking)
 - Do not mix **<=** and **=** in the same always block.

Part 2: Verilog Implementation

- Do **not** assign the same register in two different always blocks.

```
always @ (*)  
    a = b;
```


```
always @ (*)  
    a = c;
```

NO!

This should be avoided


Part 2: Verilog Implementation

- Separate three parts of the code:

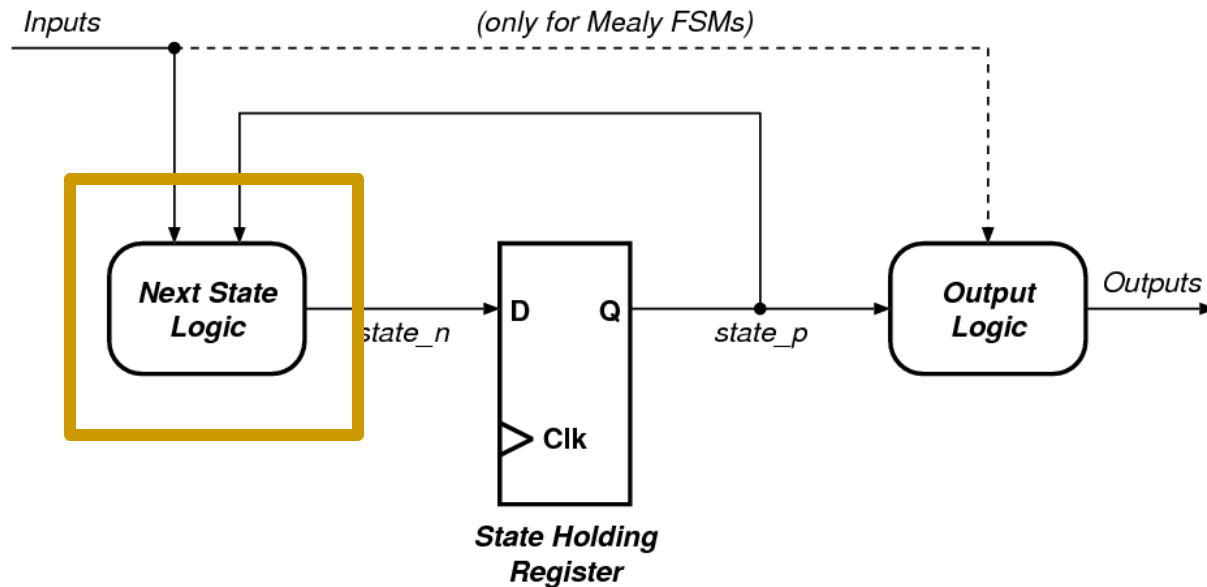

Verilog Implementation: FSM

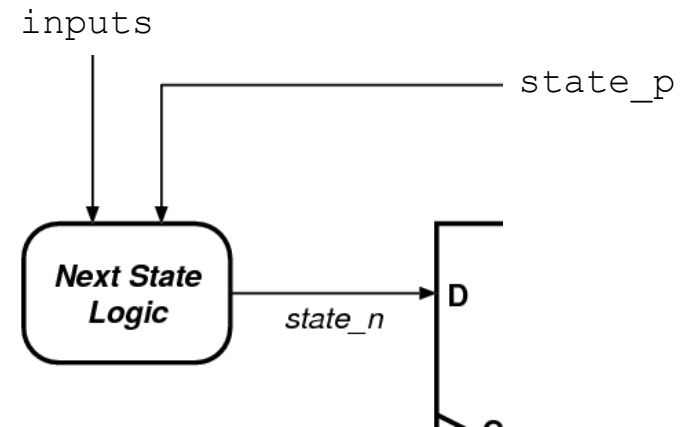- The **next state logic** determines how to transition from the **current state** to the **next state**.
 - Current state: `state_p`
 - Next state: `state_n`



```
//FSM to determine next state depending on input
always @ (posedge )
begin


    //Add next state logic here

end
```

This is the general idea and not taken from a solution


Part 2: Verilog Implementation

- Separate three parts of the code:

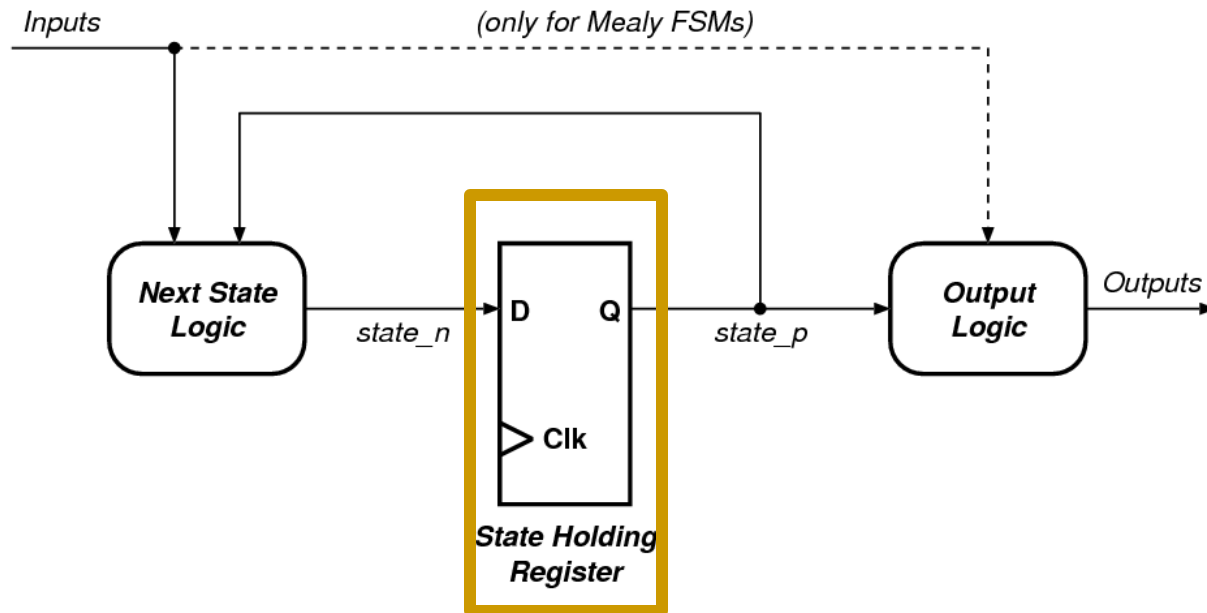


Verilog Implementation: Flip-Flops

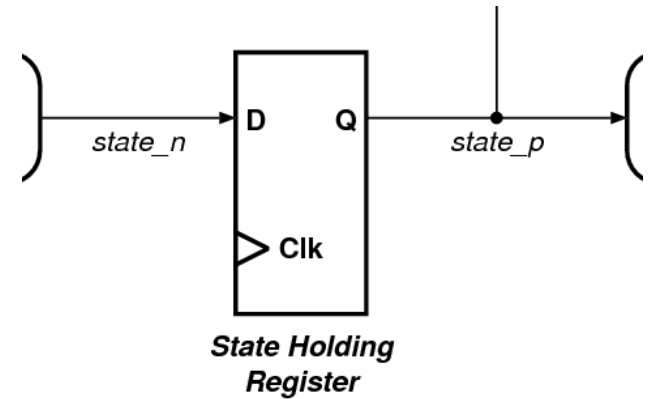- We use a **rising-clock-edge triggered flip-flop** (with reset) as a state register.
- In Verilog we use an `always` block with the **clock signal** and the **reset** signal in the **sensitivity list**.
- The **rising-clock-edge** is given to us in Verilog by `posedge`.



Verilog Implementation: Flip-Flops

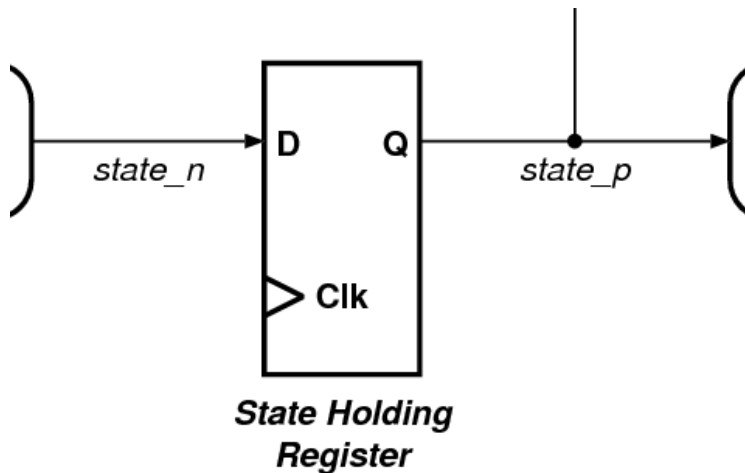


```
//State update
always @ (posedge CLK, posedge RESET)
begin
    if (RESET) state_p <= ;
    else state_p <= ;
end
```


This is the general idea and not taken from a solution

Part 2: Verilog Implementation

- Separate three parts of the code:

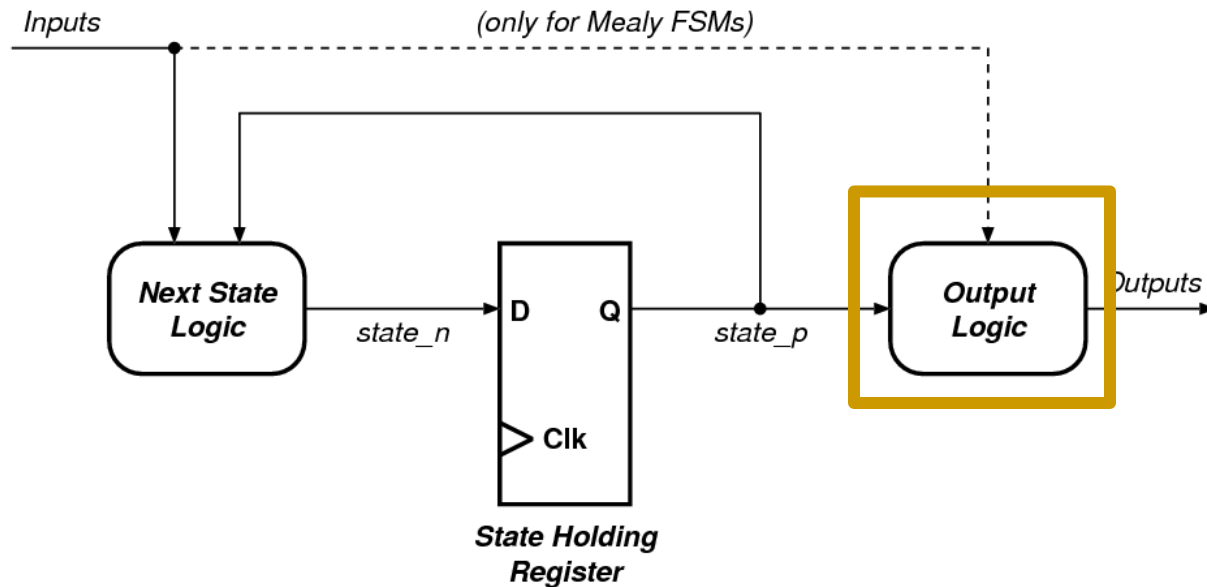

Verilog Implementation: Output Logic

 


```
//Output Logic  
assign LED = //Here you should assign the output
```

This is the general idea and not taken from a solution

Part 3: Implementing the Clock (I)

- The problem of using push-buttons as clock:
 - ❑ Compared to the speed of the FPGA the change in a push button is *very* slow (~ 1 million times slower)
 - ❑ During the slow transition, the FPGA will see many **fast occurring transitions** and would interpret each of them as a clock edge. (**Bouncing**)

 

Part 3: Implementing the Clock (II)

- **CLK100Mhz (W5):** Your board contains a 100Mhz crystal oscillator circuit.
- **Problem:** The clock is too fast.
- **Solution:** A clock divider:

```
module clk_div(input clk, input rst, output clk_en);  
    reg [24:0] clk_count;  
    always @ (posedge clk)  
        //posedge defines a rising edge (transition from 0 to 1)  
        begin  
            if (rst)  
                clk_count <= 0;  
            else  
                clk_count <= clk_count + 1;  
            end  
            assign clk_en = &clk_count;  
        endmodule
```

Verilog Implementation: Clock Design

- `&clk_count` evaluates to 1 exactly when all bits of `clk_count` are 1 and 0 otherwise.
- This is the case when we counted from 0 to $2^{25} - 1$.
 - $2^{25} - 1 = 25b'11\dots1$
 - Overflow handles the transition from $25b'1\dots1$ to $25b'0\dots0$.
- The slowed clock hence ticks every $\sim 2^{25}$ clock ticks.

```
module clk_div(input clk, input rst, output clk_en);
    reg [24:0] clk_count;
    always @ (posedge clk)
        //posedge defines a rising edge (transition from 0 to 1)
        begin
            if (rst)
                clk_count <= 0;
            else
                clk_count <= clk_count + 1;
            end
        assign clk_en = &clk_count;
    endmodule
```

Part 4: Defining the Constraints

- We must specify constraints for:
 - ❑ Buttons for control
 - ❑ LEDs for output lights
 - ❑ Connections for clock

The manual contains more information
about the constraints.

Last Words

- In Lab 4, you will **implement a finite-state machine using Verilog**.
- Design and implement a simple circuit that emulates the blinking lights of a Ford Thunderbird.
- Understand how the **clock signal is derived in the FPGA board**.
- **Write an FSM** that implements the Ford Thunderbird blinking sequence.
- In the report you will implement a **dimming function**, so that the lights are not only on and off, but can have intermediate levels

Report Deadline

[26. April 2024 23:59]

Digital Design & Computer Arch.

Lab 4 Supplement: Finite-State Machines

Frank K. Gürkaynak

Seyyedmohammad Sadrosadati

ETH Zurich

Spring 2024

[09. April 2024]