

Microarchitecture

Digital Design and Computer Architecture

Mohammad Sadrosadati

Frank K. Gürkaynak

<http://safari.ethz.ch/ddca>

In This Lecture

- Overview of the MIPS Microprocessor
- RTL Design Revisited
- Single-Cycle Processor
- Performance Analysis

Introduction

■ Microarchitecture:

- How to implement an architecture in hardware

■ Processor:

- Datapath: functional blocks
- Control: control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

Microarchitecture

- **Multiple implementations for a single architecture:**
- *Single-cycle* (this week)
 - Each instruction executes in a single cycle
- *Multicycle* (in the book, we will not cover it)
 - Each instruction is broken up into a series of shorter steps
 - One instruction is executed piece-wise
 - Allows re-use of components (ALU, memory)
- *Pipelined* (just after we finish this one)
 - Each instruction is broken up into a series of steps
 - Multiple instructions execute at once
 - Better for performance

What does our Microprocessor do ?

- **Program is in memory, stored as a series of instructions.**
- **Basic execution is:**
 - Read one instruction
 - Decode what it wants
 - Find the operands either from registers or from memory
 - Perform the operation as dictated by the instruction
 - Write the result (if necessary)
 - Go to the next instruction

What are the Basic Components of MIPS?

■ The main pieces

- Memory to store program
- Registers to access data fast
- Data memory to store more data
- An ALU to perform the core function

What are the Basic Components of MIPS?

■ The main pieces

- Memory to store program
- Registers to access data fast
- Data memory to store more data
- An ALU to perform the core function

■ Some auxiliary pieces

- A program counter to tell where to find next instruction
- Some logic to decode instructions
- A way to manipulate the program counter for branches

What are the Basic Components of MIPS?

■ The main pieces

- Memory to store program
- Registers to access data fast
- Data memory to store more data
- An ALU to perform the core function

■ Some auxiliary pieces

- A program counter to tell where to find next instruction
- Some logic to decode instructions
- A way to manipulate the program counter for branches

■ *Today we will see how it all comes together*

RTL Design Revisited

- **Registers store the current state**
- **Combinational logic determines next state**
 - Data moves from one register to another (datapath)
 - Control signals move data through the datapath
 - Control signals depend on state and input
- **Clock moves us from state to another**

Let us Start with Building the Processor

- Program is stored in a (read-only) memory as 32-bit binary values.
- Memory addresses are also 32-bit wide, allowing (in theory) $2^{32} = 4$ Gigabytes of addressed memory.
- The actual address is stored in a register called PC.

Assembly Code

```
lw    $t2, 32($0)
add   $s0, $s1, $s2
addi  $t0, $s3, -12
sub   $t0, $t3, $t5
```

Machine Code

```
0x8C0A0020
0x02328020
0x2268FFF4
0x016D4022
```

Stored Program

Address	Instructions
⋮	⋮
0040000C	0 1 6 D 4 0 2 2
00400008	2 2 6 8 F F F 4
00400004	0 2 3 2 8 0 2 0
00400000	8 C 0 A 0 0 2 0 ← PC
⋮	⋮

Main Memory

What to do with the Program Counter?

- The PC needs to be incremented by 4 during each cycle (for the time being).
- Initial PC value (after reset) is 0x00400000

```
reg [31:0] PC_p, PC_n;           // Present and next state of PC

// [...]

assign PC_n <= PC_p + 4;          // Increment by 4;

always @ (posedge clk, negedge rst)
begin
    if (rst == '0') PC_p <= 32'h00400000; // default
    else             PC_p <= PC_n;         // when clk
end
```

We have an Instruction Now What ?

- **There are different types of instructions**

- *R type* (three registers)
- *I type* (the one with immediate values)
- *J type* (for changing the flow)

- **First only a subset of MIPS instructions:**

- R type instructions: and, or, add, sub, slt
- Memory instructions: lw, sw
- Branch instructions: beq

- **Later we will add addi and j**

R-Type MIPS instructions


■ Register-type: 3 register operands:

- rs, rt: source registers
- rd: destination register

■ Other fields:

- *op*: the operation code or opcode (0 for R-type instructions)
- *funct*: the function together, the opcode and function tell the computer what operation to perform
- *shamt*: the shift amount for shift instructions, otherwise it's 0

R-Type

 

R-Type Examples

Assembly Code

```
add $s0, $s1, $s2
```

```
sub $t0, $t3, $t5
```

Field Values

op	rs	rt	rd	shamt	funct
0	17	18	16	0	32
0	11	13	8	0	34
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Machine Code

op	rs	rt	rd	shamt	funct	
000000	10001	10010	10000	00000	100000	(0x02328020)
000000	01011	01101	01000	00000	100010	(0x016D4022)
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits	

Note the order of registers in the assembly code:

add rd, rs, rt

We Need a Register File

- **Store 32 registers, each 32-bit**
 - $2^5 == 32$, we need 5 bits to address each
- **Every R-type instruction uses 3 register**
 - Two for reading (RS, RT)
 - One for writing (RD)
- **We need a special memory with:**
 - 2 read ports (address x2, data out x2)
 - 1 write port (address, data in)

Register File

```
input [4:0]    a_rs, a_rt, a_rd;
input [31:0]  di_rd;
input                we_rd;
output [31:0] do_rs, do_rt;

    reg [31:0] R_arr [31:0]; // Array that stores regs

// Circuit description
assign do_rs = R_arr[a_rs];           // Read RS

assign do_rt = R_arr[a_rt];           // Read RT

always @ (posedge clk)
    if (we_rd) R_arr[a_rd] <= di_rd; // write RD
```


Register File

```
input [4:0]    a_rs, a_rt, a_rd;
input [31:0]   di_rd;
input         we_rd;
output [31:0]  do_rs, do_rt;


reg [31:0] R_arr [31:0]; // Array that stores regs

// Circuit description; add the trick with $0
assign do_rs = (a_rs != 5'b00000)?    // is address 0?
               R_arr[a_rs] : 0;       // Read RS or 0

assign do_rt = (a_rt != 5'b00000)?    // is address 0?
               R_arr[a_rt] : 0;       // Read RT or 0


always @ (posedge clk)
    if (we_rd) R_arr[a_rd] <= di_rd; // write RD
```

ALU Does the Real Work in a Processor

 

$F_{2:0}$	Function
000	$A \& B$
001	$A \mid B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \mid \sim B$
110	$A - B$
111	SLT

Review: ALU

 

$F_{2:0}$	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & ~B
101	A ~B
110	A - B
111	SLT

So far so good

- **We have most of the components for MIPS**
 - We still do not have data memory

So far so good

- **We have most of the components for MIPS**
 - We still do not have data memory
- **We can implement all R-type instructions**
 - Assuming our ALU can handle all of the functions
 - At the moment we do not have the shifter
 - We know what to do for more functions.

So far so good

- **We have most of the components for MIPS**
 - We still do not have data memory
- **We can implement all R-type instructions**
 - Assuming our ALU can handle all of the functions
 - At the moment we do not have the shifter
 - We know what to do for more functions.
- **...but not much else**
 - *No memory access*
 - *No immediate values*
 - *No conditional branches, no absolute jumps*

Data Memory

- Will be used to store the bulk of data

```
input [15:0]  addr; // Only 16 bits in this example
input [31:0]  di;
input                we;
output [31:0] do;

reg [65535:0] M_arr [31:0];           // Array for Memory

// Circuit description
assign do = M_arr[addr];              // Read memory

always @ (posedge clk)
    if (we) M_arr[addr] <= di;        // write memory
```

Let us Read (then Write) to Memory

- **The main memory can have up to 2^{32} bytes**
 - It needs an 32-bit address for the entire memory.
 - In practice much smaller memories are used
- **We need the `lw` instruction to read from memory**
 - I-type instruction
 - We need to calculate the address from an immediate value and a register.
 - Maybe we can use the ALU to add immediate to the register?

I-Type

■ Immediate-type: 3 operands:

- rs, rt: register operands
- imm: 16-bit two's complement immediate

■ Other fields:

- *op*: the opcode
- Simplicity favors regularity: all instructions have opcode
- Operation is completely determined by the opcode

I-Type



Differences between R-type and I-type

■ Changes to Register file

- *RS + sign extended immediate* is the address
- RS is always read.
- For some instructions RT is read as well
- If one register is written it is RT, not RD
- The write_data_in can come from Memory or ALU
- Not all I-type instructions write to register file

■ Changes to ALU

- Used to calculate memory address, add function needed during non R-type operations
- Result is also used as address for the data memory
- One input is no longer RT, but the immediate value

Now Writing to Memory is Similar

- We need the **SW** instruction to write to memory
 - I-type instruction
 - Address calculated the same way
 - Unlike, previous step, there is no writing back to register.
 - But we need to enable the write enable of the memory

Our MIPS Datapath has Several Options

- **ALU inputs**
 - Either RT or Immediate
- **Write Address of Register File**
 - Either RD or RT
- **Write Data In of Register File**
 - Either ALU out or Data Memory Out
- **Write enable of Register File**
 - Not always a register write
- **Write enable of Memory**
 - Only when writing to memory (sw)

Our MIPS Datapath has Several Options

- **ALU inputs**
 - Either RT or Immediate (*MUX*)
- **Write Address of Register File**
 - Either RD or RT (*MUX*)
- **Write Data In of Register File**
 - Either ALU out or Data Memory Out (*MUX*)
- **Write enable of Register File**
 - Not always a register write (*MUX*)
- **Write enable of Memory**
 - Only when writing to memory (sw) (*MUX*)

All these options are our control signals

Let us Develop our Control Table

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	MemWrite	MemtoReg	ALUOp

- **RegWrite:** Write enable for the register file
- **RegDst:** Write to register RD or RT
- **AluSrc:** ALU input RT or immediate
- **MemWrite:** Write Enable
- **MemtoReg:** Register data in from Memory or ALU
- **ALUOp:** What operation does ALU do

Let us Develop our Control Table

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	funct

- **RegWrite:** Write enable for the register file
- **RegDst:** Write to register RD or RT
- **AluSrc:** ALU input RT or immediate
- **MemWrite:** Write Enable
- **MemtoReg:** Register data in from Memory or ALU
- **ALUOp:** What operation does ALU do

Let us Develop our Control Table

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	funct
lw	100011	1	0	1	0	1	add

- **RegWrite:** Write enable for the register file
- **RegDst:** Write to register RD or RT
- **AluSrc:** ALU input RT or immediate
- **MemWrite:** Write Enable
- **MemtoReg:** Register data in from Memory or ALU
- **ALUOp:** What operation does ALU do

Let us Develop our Control Table

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	funct
lw	100011	1	0	1	0	1	add
sw	101011	0	X	1	1	X	add

- **RegWrite:** Write enable for the register file
- **RegDst:** Write to register RD or RT
- **AluSrc:** ALU input RT or immediate
- **MemWrite:** Write Enable
- **MemtoReg:** Register data in from Memory or ALU
- **ALUOp:** What operation does ALU do

Now we are much better

- **We have almost all components for MIPS**
- **We already had (nearly) all R-type instructions**
 - Our ALU can implement some functions
 - We know what to do for more functions.
- **Now we can also Read and Write to memory**
- **Conditional Branches are still missing**
 - Until now, PC just increases by 4 every time.
 - We need to somehow be able to influence this.

Branch if equal: BEQ

■ From Appendix B:

Opcode: 000100

If ($[rs] == [rt]$) PC = BTA

BTA = Branch Target Address
 = PC+4 + (SignImm << 2)

Branch if equal: BEQ

- **From Appendix B:**

Opcode: 000100

If ($[rs] == [rt]$) PC = BTA

BTA = Branch Target Address
= PC+4 + (SignImm << 2)

- **We need ALU for comparison**

- Subtract RS – RT
- We need a 'zero' flag, if RS equals RT

Branch if equal: BEQ

- **From Appendix B:**

Opcode: 000100

If ($[rs] == [rt]$) PC = BTA

BTA = Branch Target Address
= PC+4 + (SignImm << 2)

- **We need ALU for comparison**

- Subtract RS – RT
- We need a 'zero' flag, if RS equals RT

- **We also need a *Second Adder***

- The immediate value has to be added to PC+4

Branch if equal: BEQ

- **From Appendix B:**

Opcode: 000100

If ($[rs] == [rt]$) PC = BTA

BTA = Branch Target Address
= PC+4 + (SignImm << 2)

- **We need ALU for comparison**

- Subtract RS – RT
- We need a 'zero' flag, if RS equals RT

- **We also need a *Second Adder***

- The immediate value has to be added to PC+4

- **PC has now two options**

- Either PC+4 or the new BTA

More Control Signals

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	0	funct
lw	100011	1	0	1	0	0	1	add
sw	101011	0	X	1	0	1	X	add
beq	000100	0	X	0	1	0	X	sub

■ New Control Signal

- **Branch:** Are we jumping or not ?

We are almost done


- **We have almost all components for MIPS**
- **We already had (nearly) all R-type instructions**
 - Our ALU can implement some functions
 - We know what to do for more functions.
- **Now we can also Read and Write to memory**
- **We also have conditional branches**
- **Absolute jumps are still missing**
 - J-type instructions
 - The next PC address is directly determined

Machine Language: J-Type

■ Jump-type

- 26-bit address operand (addr)
- Used for jump instructions (j)

J-Type

 


JTA 0000 0000 0100 0000 0000 0000 1010 0000 (0x004000A0)


26-bit addr 0000 0000 0100 0000 0000 0000 1010 0000 (0x0100028)

0 1 0 0 0 2 8

Field Values

 

Machine Code

 

Jump: J

- **From Appendix B:**

Opcode: 000010

PC = JTA

JTA = Jump Target Address
= $\{(PC+4)[31:28], \text{addr}, 2'b0\}$

- **No need for ALU**

- Assemble the JTA from PC and 26-bit immediate

- **No need for memory, register file**

- **One more option (mux + control signal) for PC**

Even More Control Signals

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp	Jump
R-type	000000	1	1	0	0	0	0	funct	0
lw	100011	1	0	1	0	0	1	add	0
sw	101011	0	X	1	0	1	X	add	0
beq	000100	0	X	0	1	0	X	sub	0
j	000010	0	X	X	X	0	X	X	1

■ New Control Signal

- *Jump*: Direct jump yes or no

Now we are Almost Done

- **We have all major parts**
 - We can implement, R, I, J type instructions
 - We can calculate, branch, and jump
 - We would be able to run most programs

Now we are Almost Done

■ We have all major parts

- We can implement, R, I, J type instructions
- We can calculate, branch, and jump
- We would be able to run most programs


■ Still we can improve:

- ALU can be improved for more 'funct'
- We do not have a shifter.
- Or a multiplier.
- More I-type functions (only lw and sw supported)
- More J-type functions (jal, jr)

Now the original slides once again

- **The following slides will repeat what we just did**
- **Consistent with the text book**

MIPS State Elements

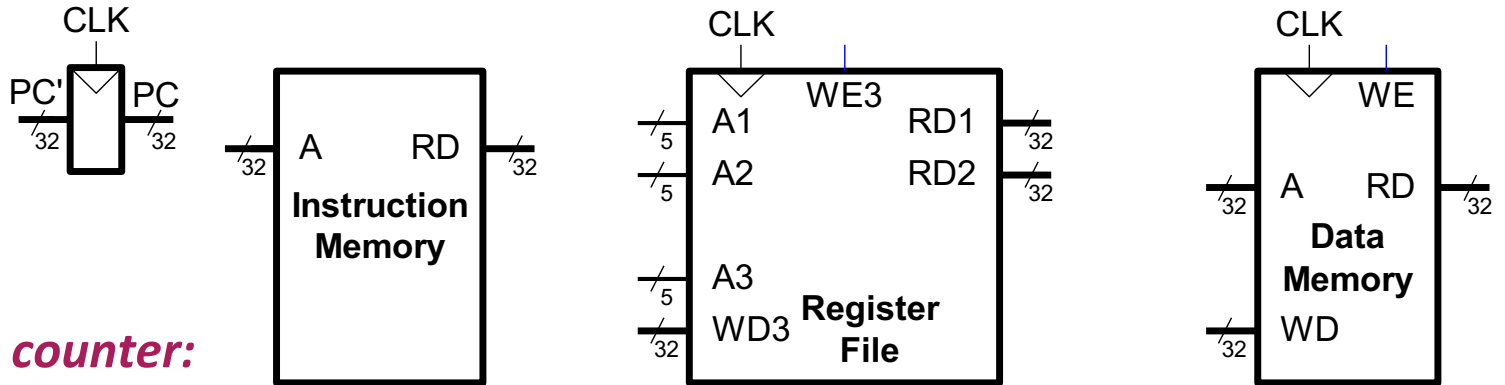

- **Program counter:**

32-bit register

- **Instruction memory:**

Takes input 32-bit address A and reads the 32-bit data (i.e., instruction) from that address to the read data output RD.

- **Register file:**


The 32-element, 32-bit register file has 2 read ports and 1 write port

- **Data memory:**

Has a single read/write port. If the write enable, WE, is 1, it writes data WD into address A on the rising edge of the clock. If the write enable is 0, it reads address A onto RD.


Single-Cycle Datapath: lw fetch

■ **STEP 1:** Fetch instruction

 


`lw $s3, 1($0) # read memory word 1 into $s3`

I-Type

 


Single-Cycle Datapath: lw register read

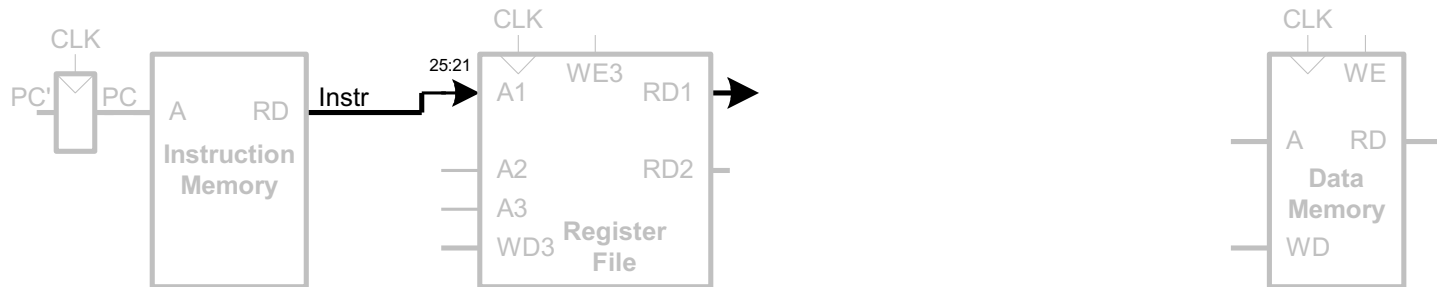- **STEP 2:** Read source operands from register file




`lw $s3, 1($0) # read memory word 1 into $s3`

I-Type

 

Single-Cycle Datapath: lw immediate

■ **STEP 3:** Sign-extend the immediate

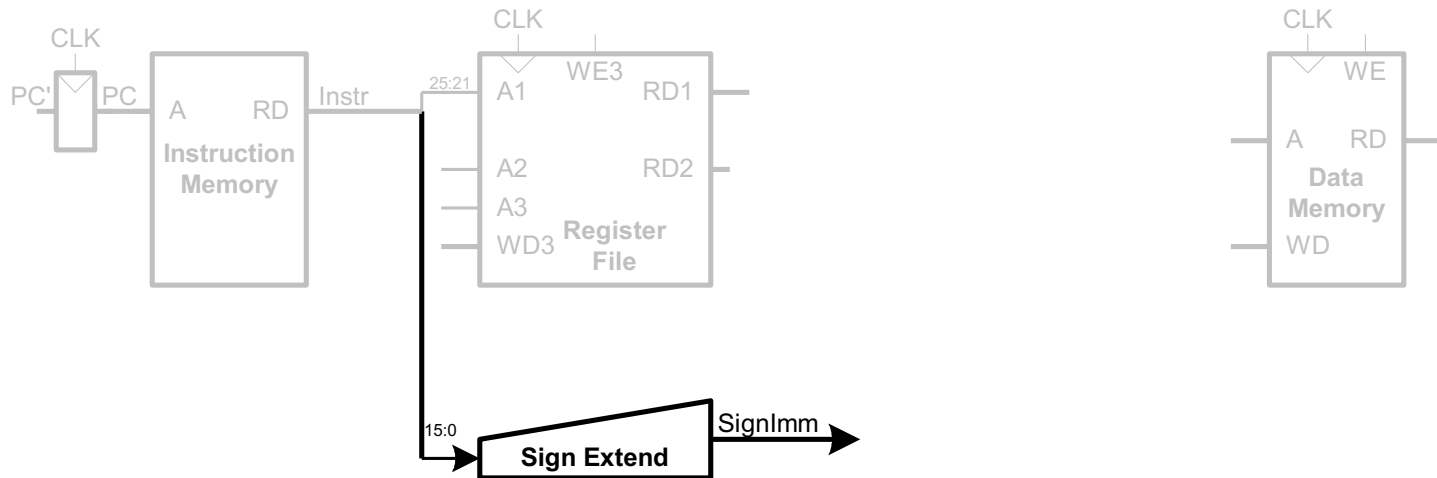


`lw $s3, 1($0) # read memory word 1 into $s3`

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

Single-Cycle Datapath: lw address

■ **STEP 4:** Compute the memory address

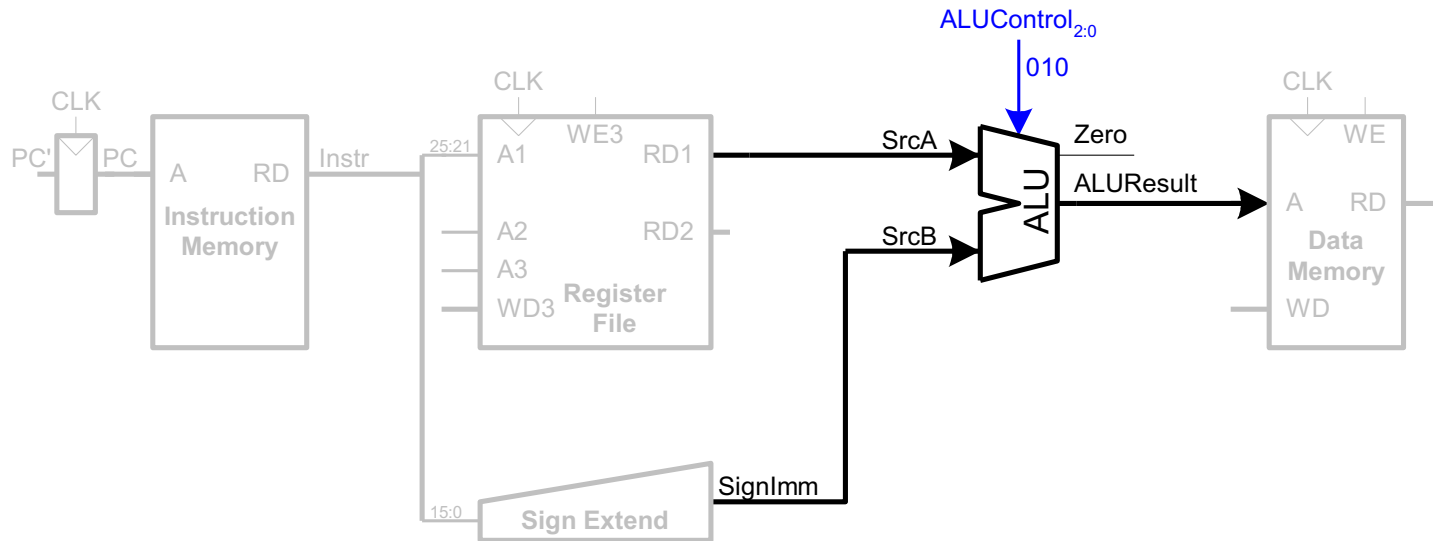


`lw $s3, 1($0) # read memory word 1 into $s3`

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

Single-Cycle Datapath: lw memory read

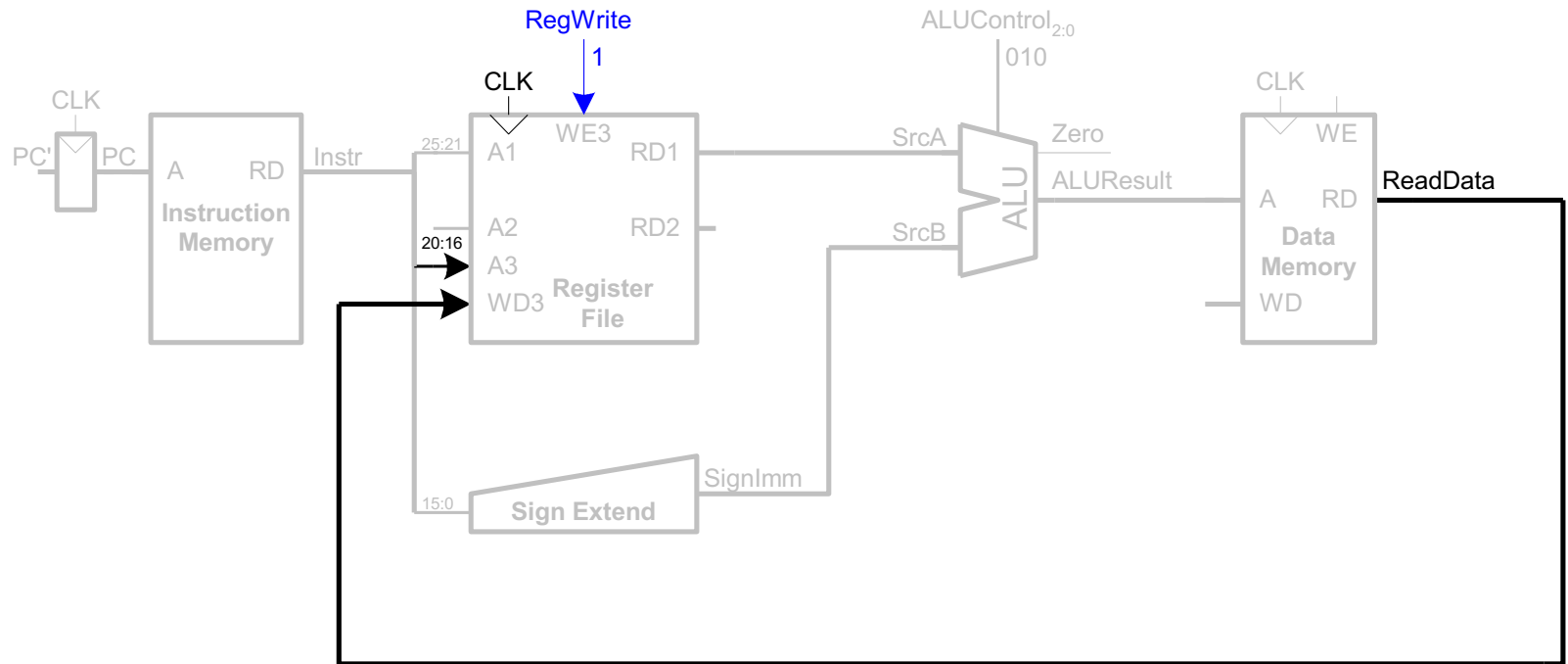■ **STEP 5:** Read from memory and write back to register file




`lw $s3, 1($0) # read memory word 1 into $s3`

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

Single-Cycle Datapath: lw PC increment

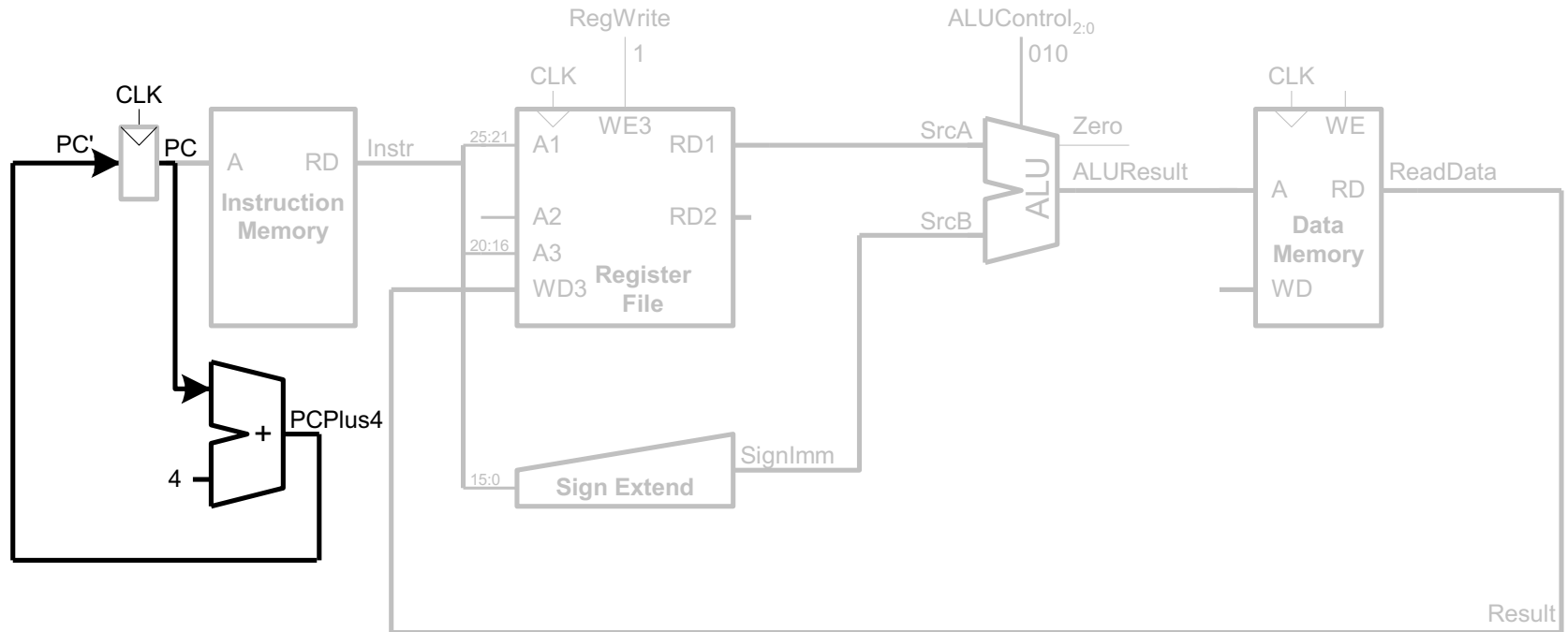■ STEP 6: Determine address of next instruction




`lw $s3, 1($0) # read memory word 1 into $s3`

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

Single-Cycle Datapath: sw

■ Write data in rt to memory

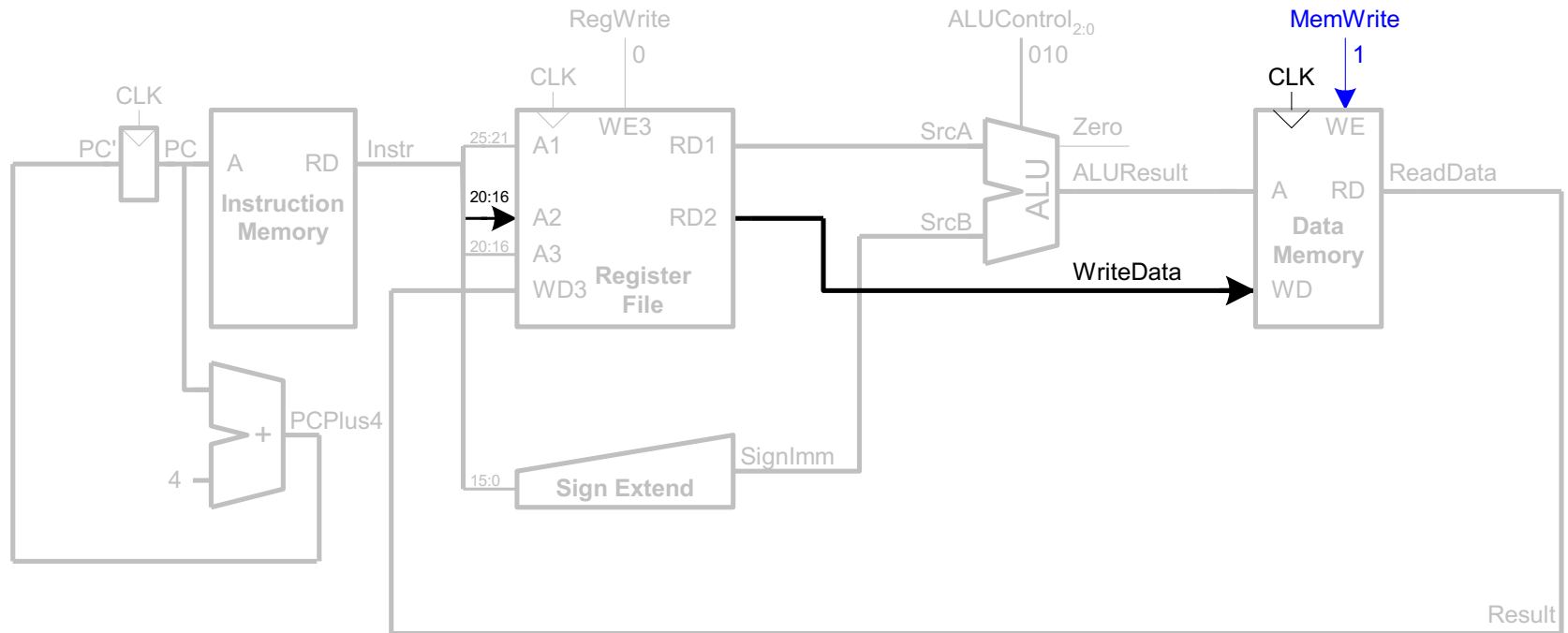


`sw $t7, 44($0) # write t7 into memory address 44`

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

Single-Cycle Datapath: R-type Instructions

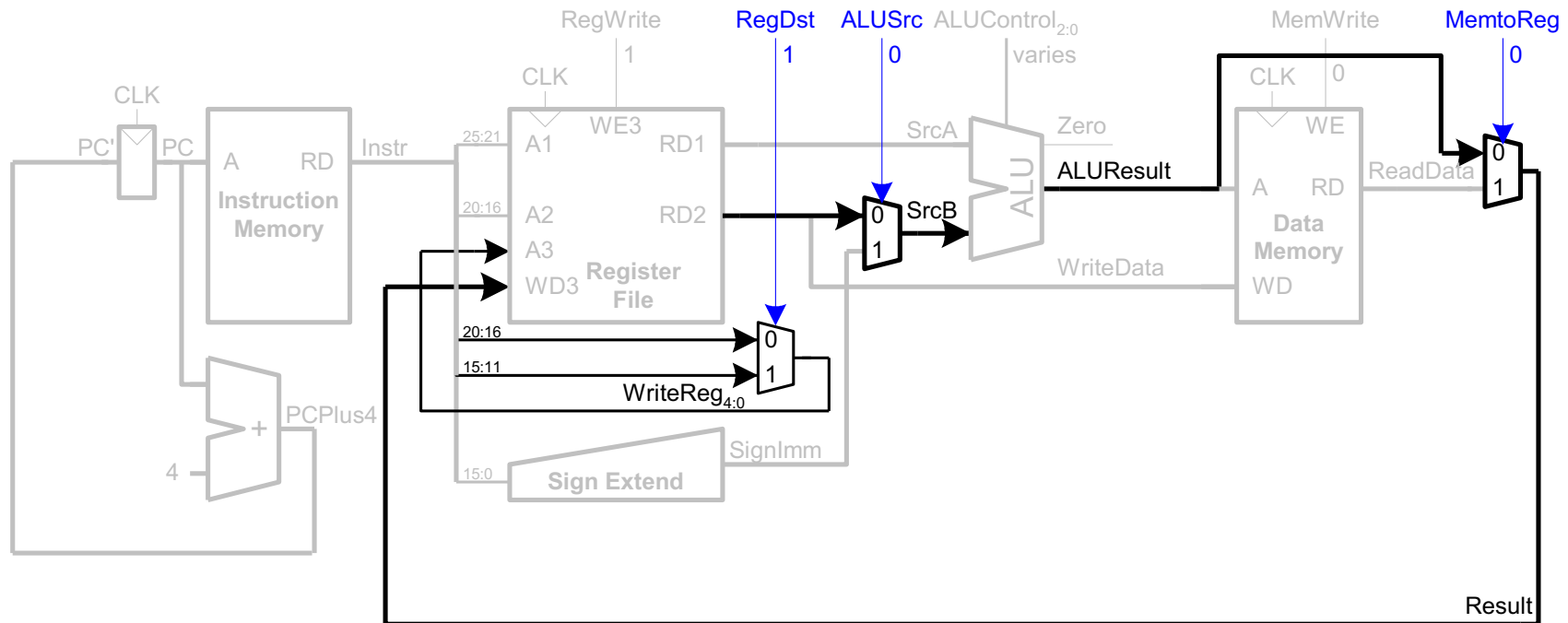- Read from rs and rt, write ALUResult to register file




add t, b, c # t = b + c

R-Type

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits


Single-Cycle Datapath: beq

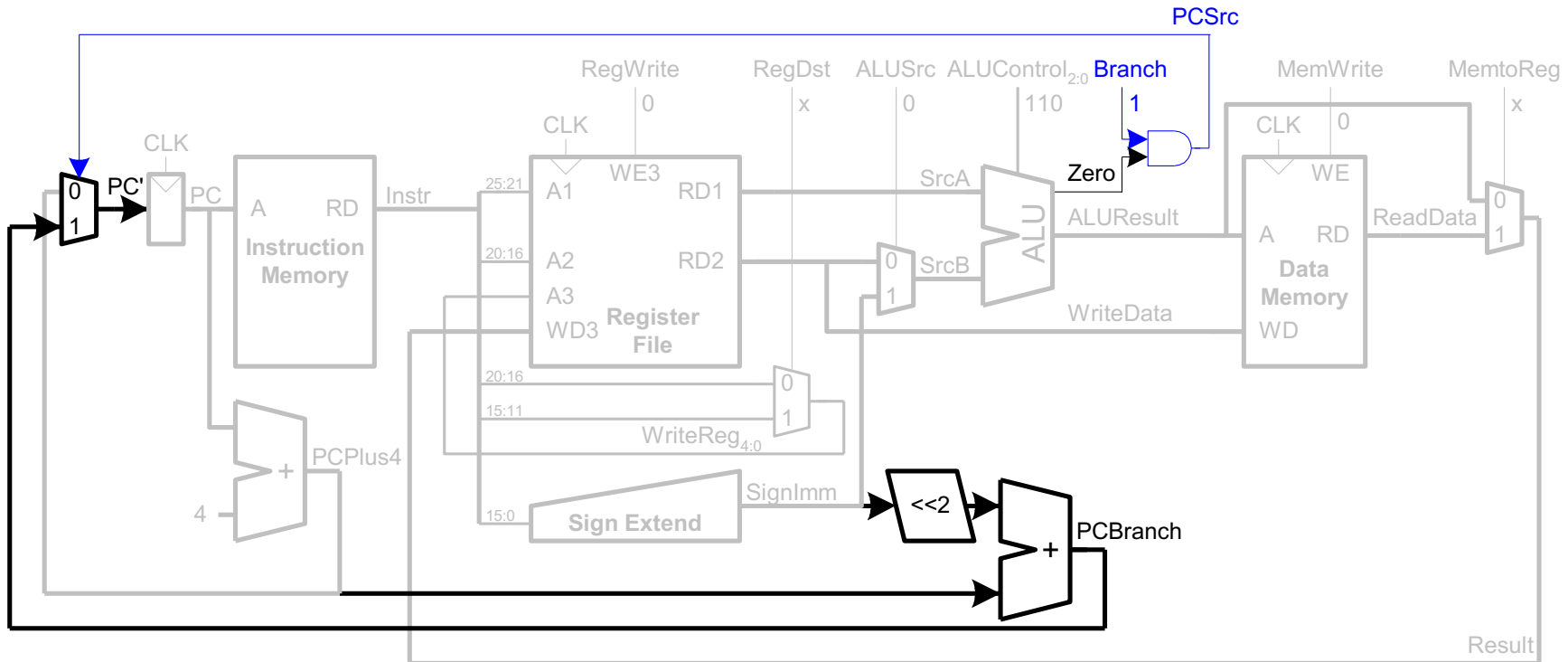


`beq $s0, $s1, target` # branch is taken

- Determine whether values in `rs` and `rt` are equal
Calculate $BTA = (\text{sign-extended immediate} \ll 2) + (PC+4)$

Complete Single-Cycle Processor

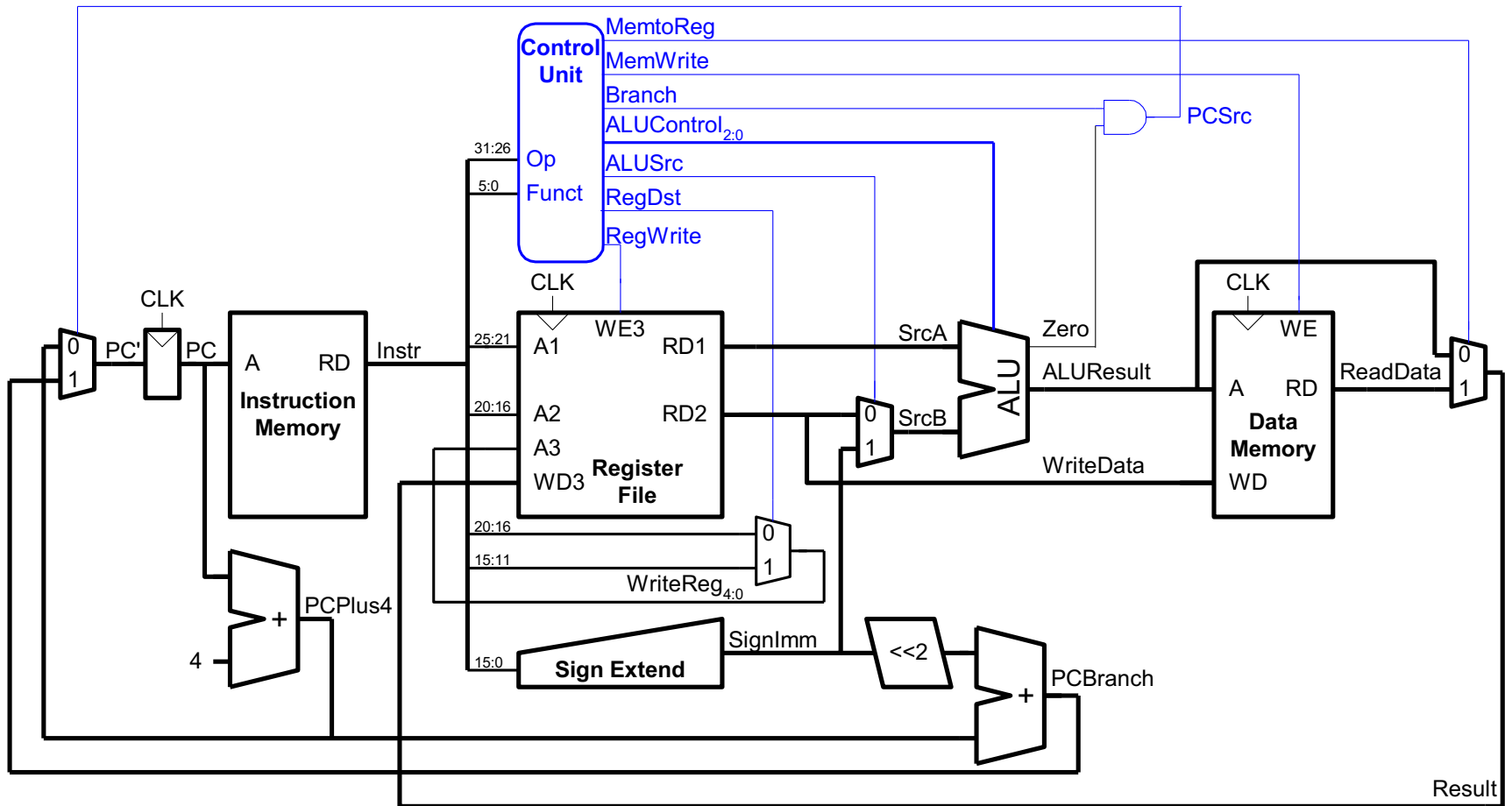


Control Unit

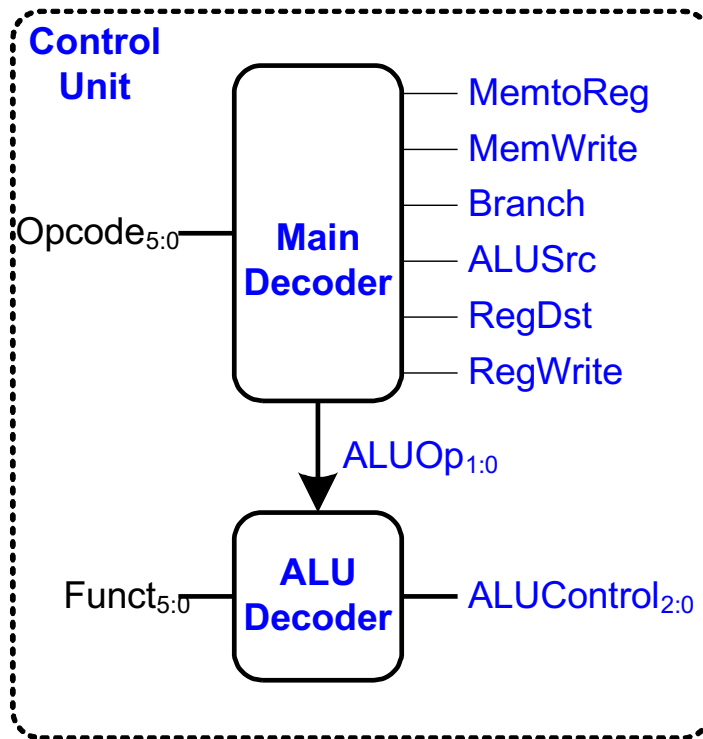


ALUOp	Meaning
00	add
01	subtract
10	look at funct field
11	n/a

ALU Does the Real Work in a Processor

 


$F_{2:0}$	Function
000	$A \& B$
001	$A \mid B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \mid \sim B$
110	$A - B$
111	SLT

Review: ALU

 

$F_{2:0}$	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & \sim B
101	A \sim B
110	A - B
111	SLT

Control Unit: ALU Decoder

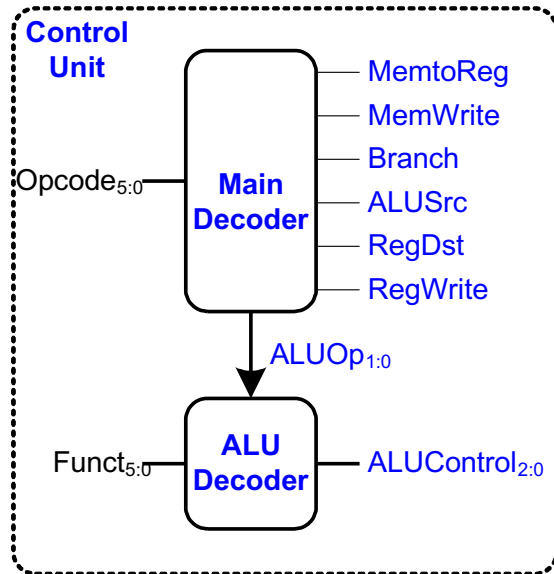


ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used


ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

Control Unit: Main Decoder


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

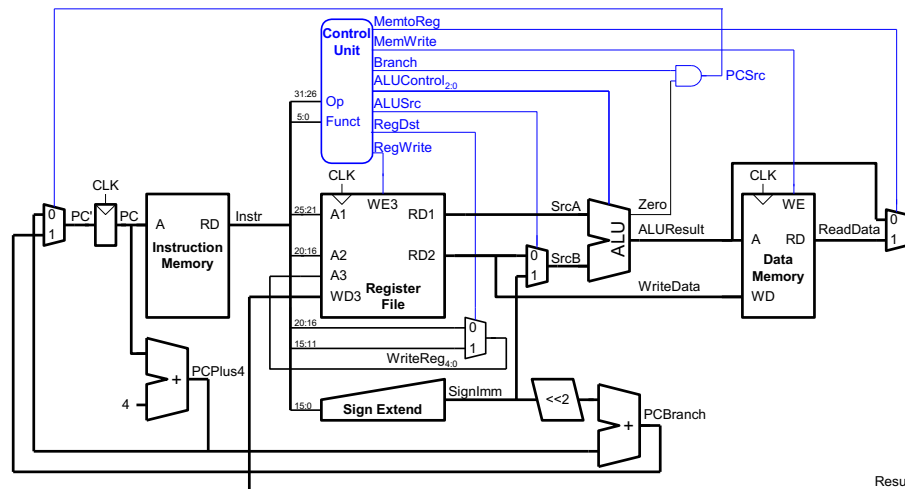

Single-Cycle Datapath Example: or

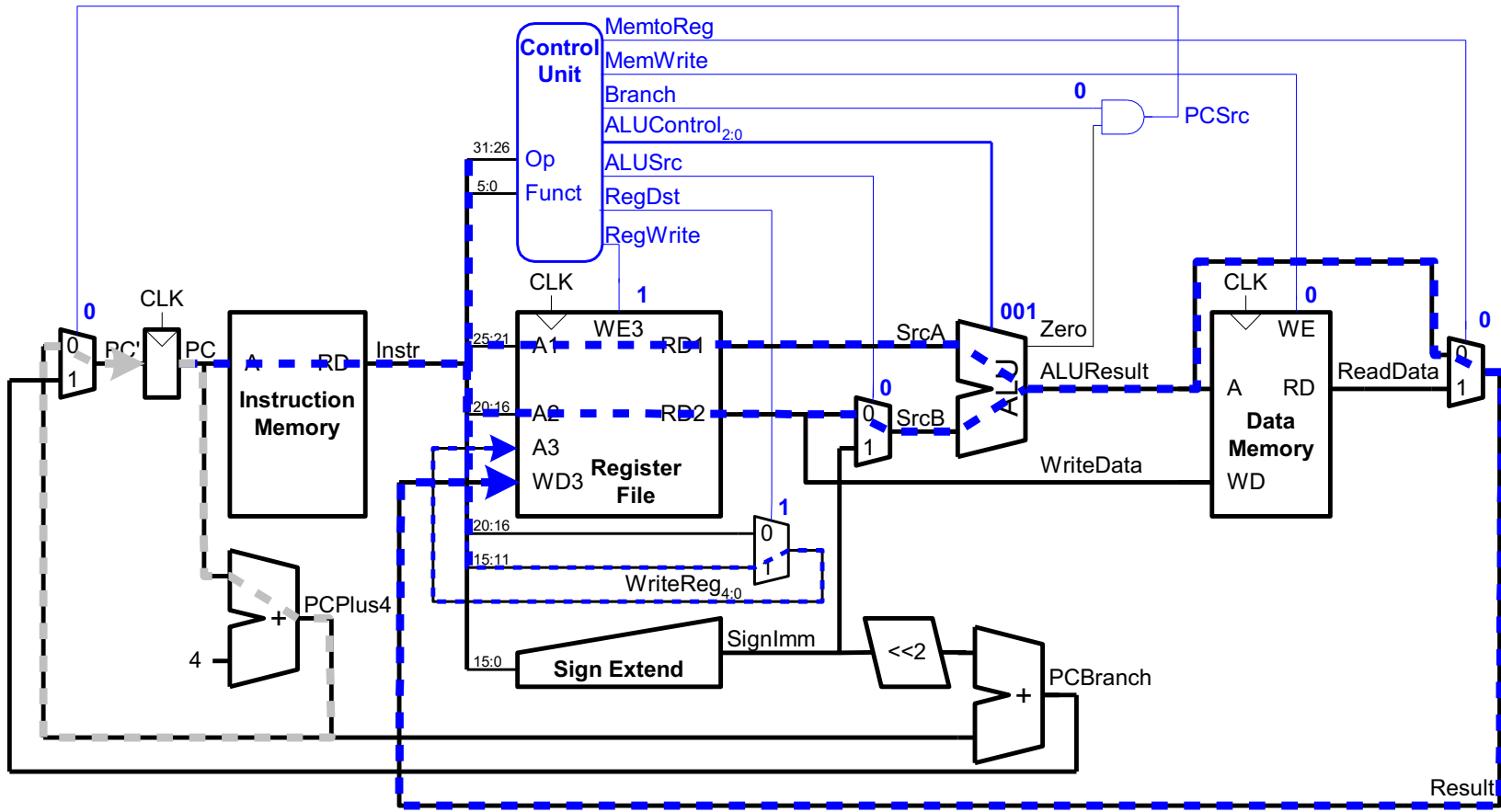

Extended Functionality: addi

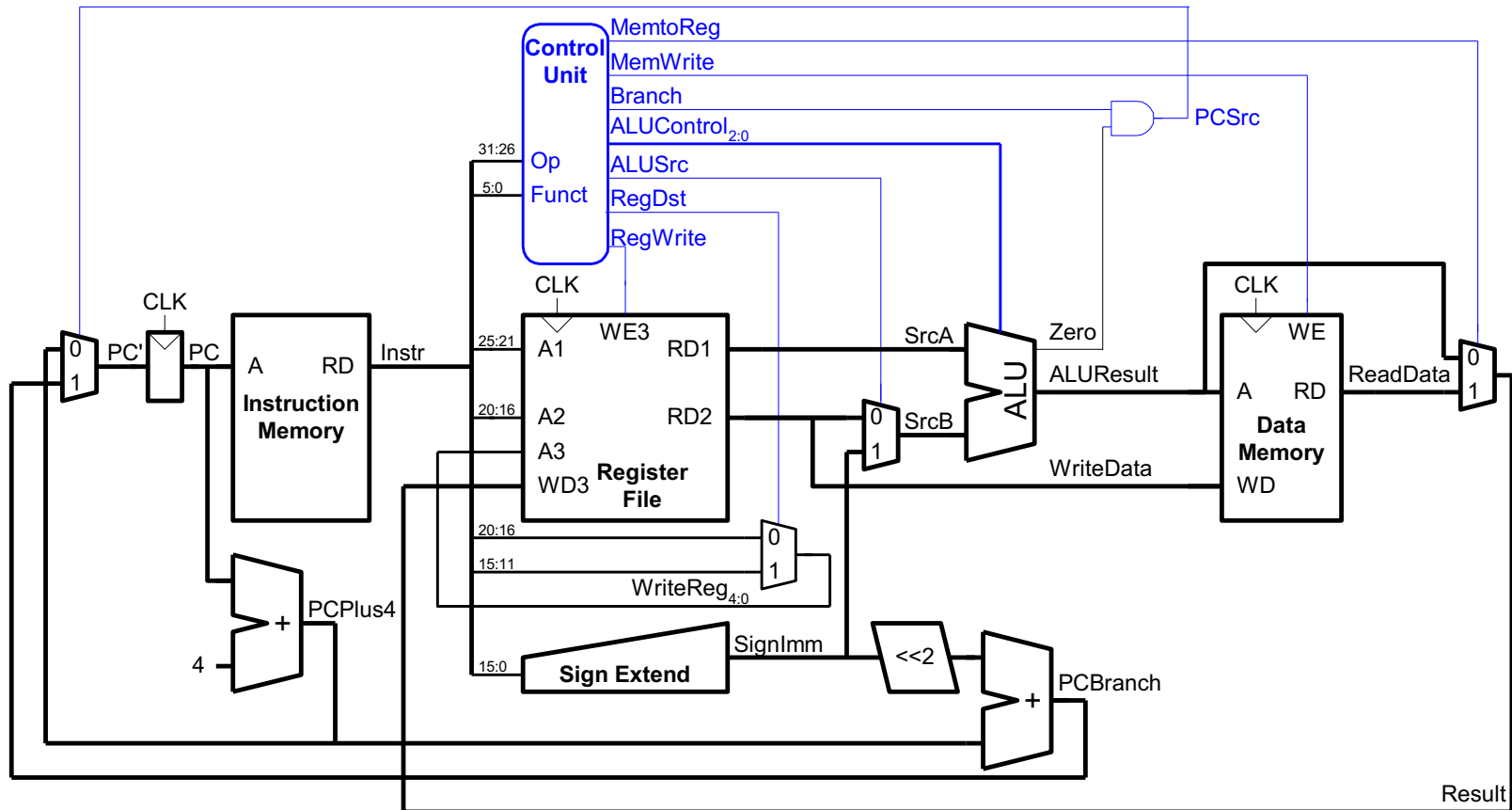


■ No change to datapath

Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00

Extended Functionality: j

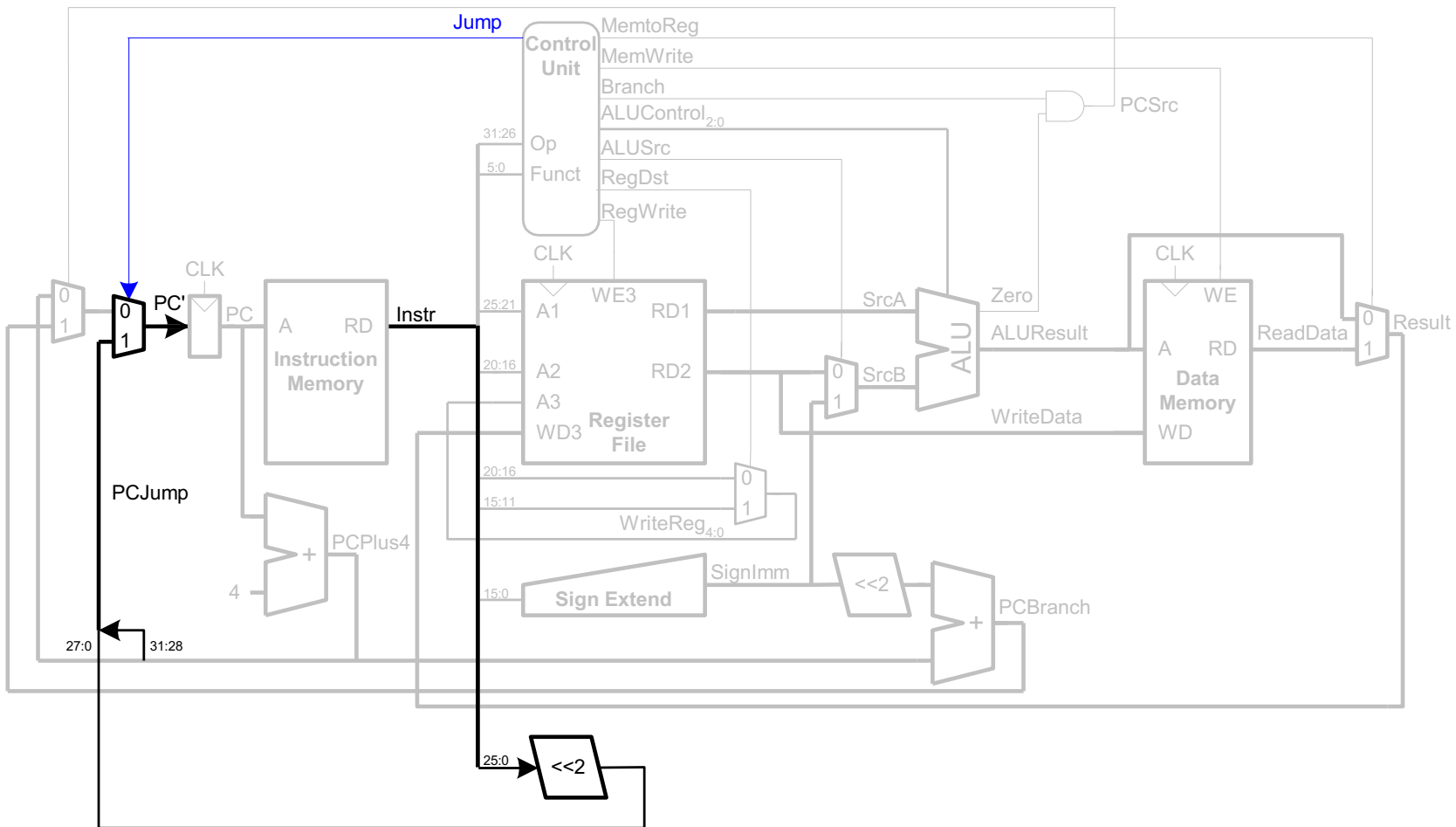

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000100	0	X	X	X	0	X	XX	1

Processor Performance

- **How fast is my program?**
 - Every program consists of a series of instructions
 - Each instruction needs to be executed.

Processor Performance

■ How fast is my program?

- Every program consists of a series of instructions
- Each instruction needs to be executed.

■ So how fast are my instructions ?

- Instructions are realized on the hardware
- They can take one or more clock cycles to complete
- *Cycles per Instruction = CPI*

Processor Performance

■ How fast is my program?

- Every program consists of a series of instructions
- Each instruction needs to be executed.

■ So how fast are my instructions ?

- Instructions are realized on the hardware
- They can take one or more clock cycles to complete
- *Cycles per Instruction = CPI*

■ How much time is one clock cycle?

- The critical path determines how much time one cycle requires = *clock period*.
- $1/\text{clock period} = \text{clock frequency}$ = how many cycles can be done each second.

Processor Performance

■ Now as a general formula

- Our program consists of executing **N** instructions.
- Our processor needs **CPI** cycles for each instruction.
- The maximum clock speed of the processor is **f**,
and the clock period is therefore **$T=1/f$**

Processor Performance

■ Now as a general formula

- Our program consists of executing **N** instructions.
- Our processor needs **CPI** cycles for each instruction.
- The maximum clock speed of the processor is **f**,
and the clock period is therefore **T=1/f**

■ Our program will execute in

$$\mathbf{N \times CPI \times (1/f) = N \times CPI \times T \text{ seconds}}$$

How can I Make the Program Run Faster?

$$N \times \text{CPI} \times (1/f)$$

How can I Make the Program Run Faster?

$$N \times \text{CPI} \times (1/f)$$

- **Reduce the number of instructions**
 - Make instructions that 'do' more (CISC)
 - Use better compilers

How can I Make the Program Run Faster?

$$N \times \text{CPI} \times (1/f)$$

- **Reduce the number of instructions**
 - Make instructions that 'do' more (CISC)
 - Use better compilers
- **Use less cycles to perform the instruction**
 - Simpler instructions (RISC)
 - Use multiple units/ALUs/cores in parallel


How can I Make the Program Run Faster?

$$N \times \text{CPI} \times (1/f)$$

- **Reduce the number of instructions**
 - Make instructions that 'do' more (CISC)
 - Use better compilers
- **Use less cycles to perform the instruction**
 - Simpler instructions (RISC)
 - Use multiple units/ALUs/cores in parallel
- **Increase the clock frequency**
 - Find a 'newer' technology to manufacture
 - Redesign time critical components
 - Adopt pipelining

Single-Cycle Performance

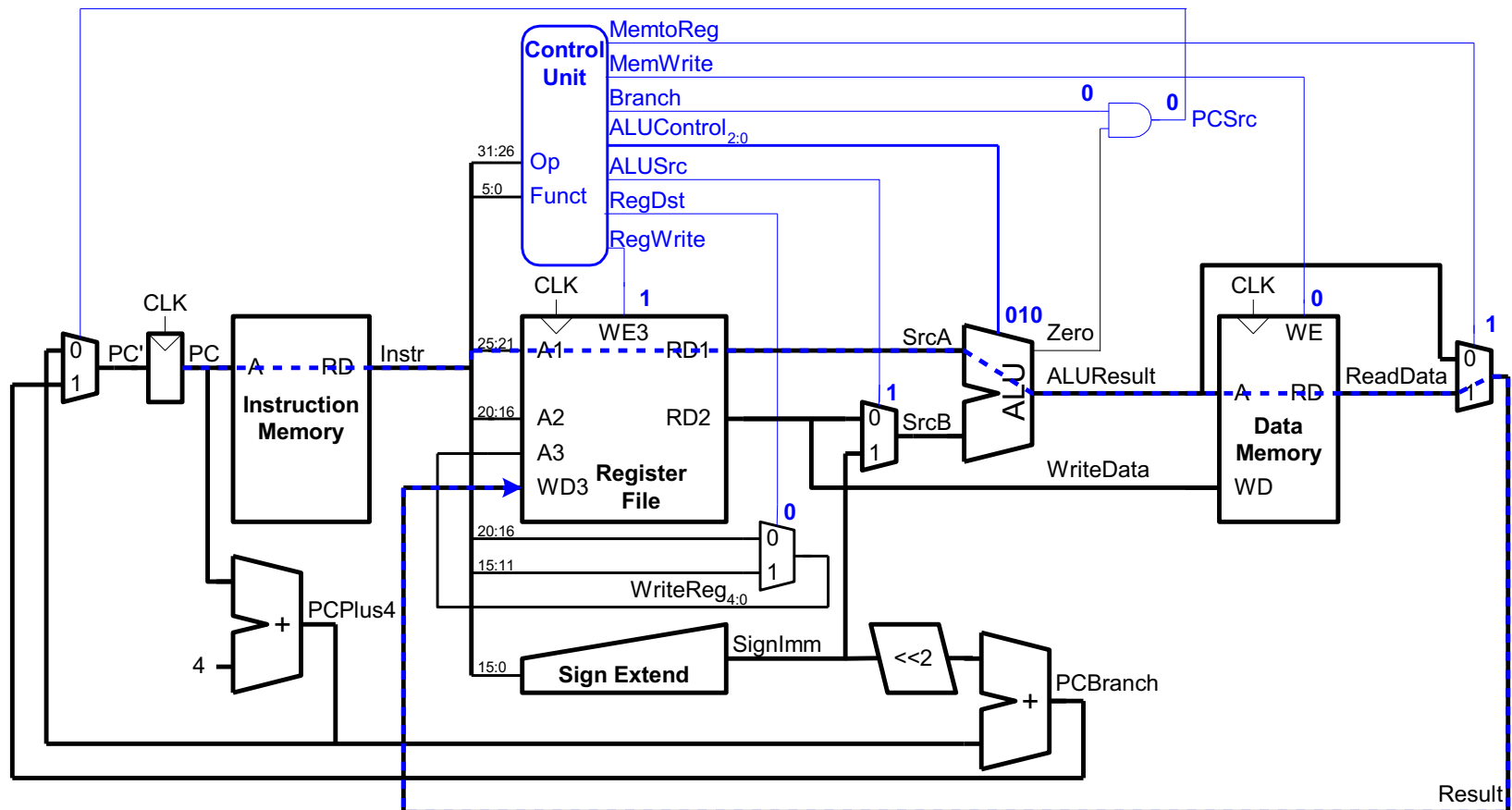- T_c is limited by the critical path (1w)



Single-Cycle Performance


■ Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

■ In most implementations, limiting paths are:

- memory, ALU, register file.
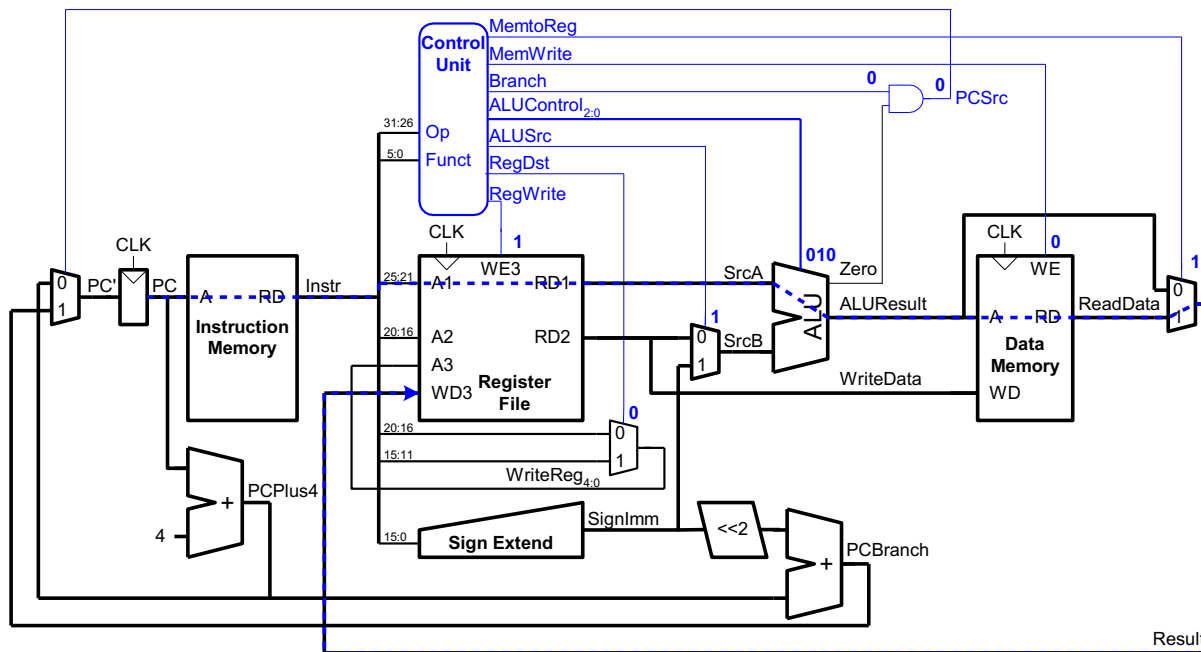
$$T_c = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$$



Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$T_c =$$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\&= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\&= 925 \text{ ps}\end{aligned}$$

Single-Cycle Performance Example

■ Example:

For a program with 100 billion instructions executing on a single-cycle MIPS processor:

Single-Cycle Performance Example

■ Example:

For a program with 100 billion instructions executing on a single-cycle MIPS processor:

$$\begin{aligned}\textit{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times \text{TC} \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= 92.5 \text{ seconds}\end{aligned}$$

What Did We Learn?

- **How to determine the performance of processors**

- CPI
- Clock speed
- Number of instructions

- **Single-cycle MIPS architecture**

- Learned individual components
 - ALU
 - Data Memory
 - Instruction Memory
 - Register File
- Discussed implementation of some instructions
- Explained the control flow