

# Sequential Circuits: Timing

Digital Design and Computer Architecture

Mohammad Sadrosadati

Frank K. Gürkaynak

<http://safari.ethz.ch/ddca>

# What will we learn?


- **Timing of Sequential Logic**
  - Setup time
  - Hold time
- **Clock frequency**
- **Metastability and prevention**

# Timing

- Flip-flop samples D at clock edge
- D must be stable when it is sampled
- Similar to a photograph, D must be stable around the clock edge
- If D is changing when it is sampled, *metastability* can occur
  - Recall that a flip-flop copies the input D to the output Q on the rising edge of the clock. This process is called sampling D on the clock edge. If D is stable at either 0 or 1 when the clock rises, this behavior is clearly defined. But what happens if D is changing at the same time the clock rises?

 
# Input Timing Constraints

- **Setup time:**  $t_{\text{setup}}$  = time before the clock edge that data must be stable (i.e. not changing)
- **Hold time:**  $t_{\text{hold}}$  = time after the clock edge that data must be stable
- **Aperture time:**  $t_a$  = time around clock edge that data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )



 
# Output Timing Constraints

- **Propagation delay:**  $t_{pcq}$  = time after clock edge that the output Q is guaranteed to be stable (i.e., to stop changing)
- **Contamination delay:**  $t_{ccq}$  = time after clock edge that Q might be unstable (i.e., start changing)



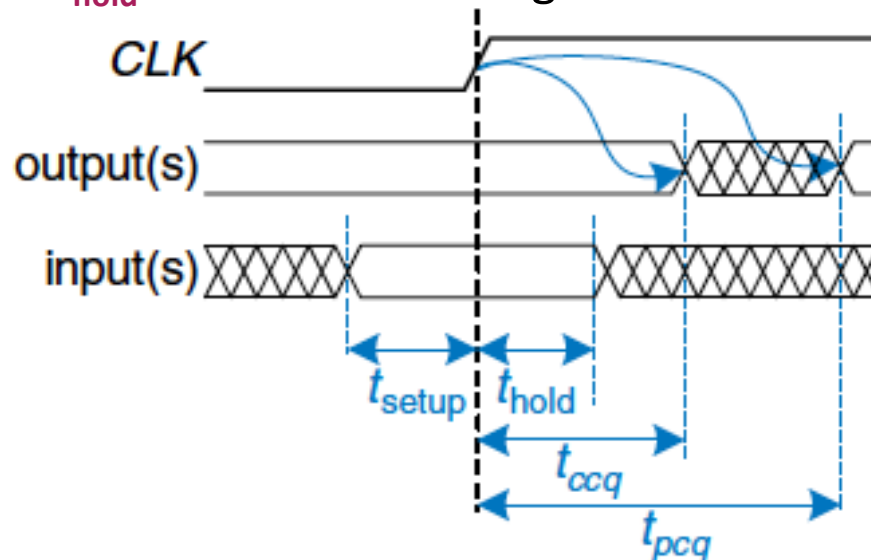
# Dynamic Discipline

- The input to a synchronous sequential circuit must be stable during the aperture (setup and hold) time around the clock edge.
- Specifically, the input must be stable
  - at least  $t_{\text{setup}}$  before the clock edge
  - at least until  $t_{\text{hold}}$  after the clock edge


 
# Dynamic Discipline

- The delay between registers has a minimum and maximum delay, dependent on the delays of the circuit elements




# Setup Time Constraint

- The clock period or cycle time,  $T_c$ , is the time between rising edges of a repetitive clock signal. Its reciprocal,  $f_c=1/T_c$ , is the clock frequency.
- All else being the same, increasing the clock frequency increases the work that a digital system can accomplish per unit time.
- Frequency is measured in units of Hertz (Hz), or cycles per second:
  - 1 megahertz (MHz)  $10^6$  Hz
  - 1 gigahertz (GHz)  $10^9$  Hz.



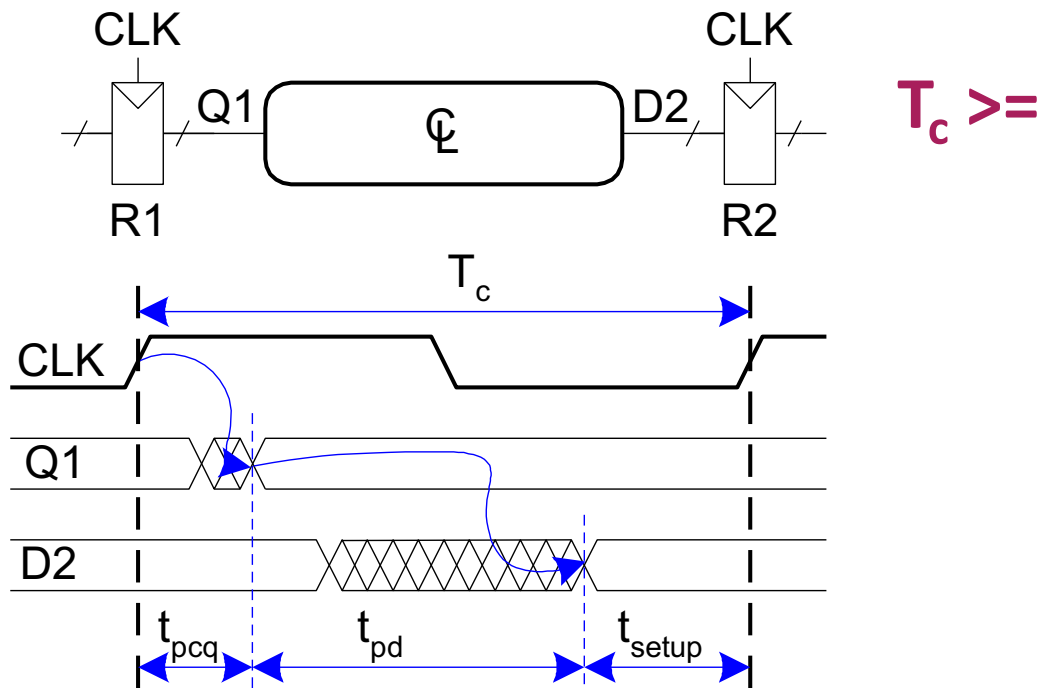
# Setup Time Constraint

- The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.


 
# Setup Time Constraint

- The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.




$$T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$

$$t_{\text{pd}} \leq$$
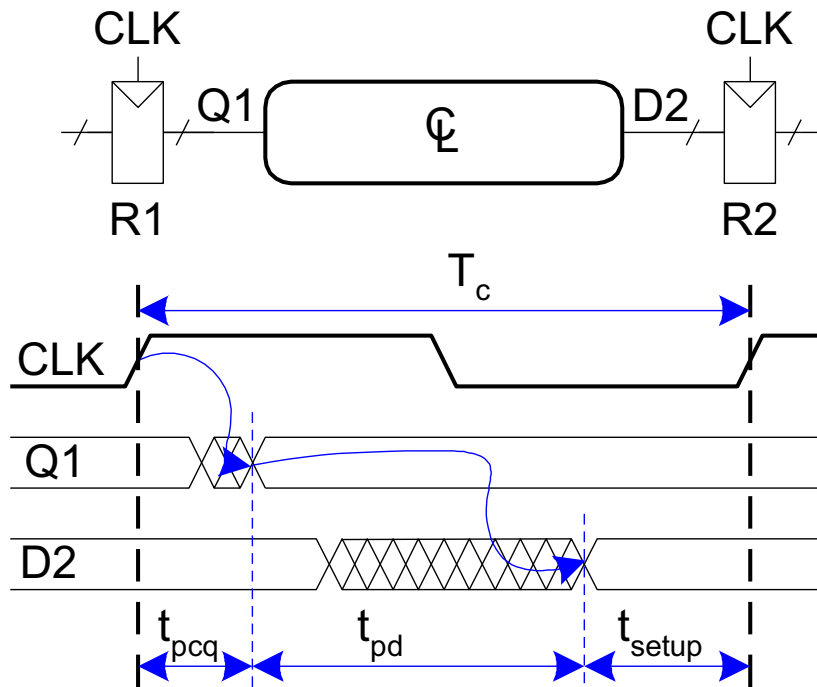
# Setup Time Constraint

- The setup time constraint depends on the maximum delay from register R1 through the combinational logic.
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before the clock edge.




$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$
 
# Hold Time Constraint


- The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$t_{\text{hold}} <$
 
# Hold Time Constraint


- The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} >$$

 
# Hold Time Constraint

- The hold time constraint depends on the minimum delay from register R1 through the combinational logic.
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge.



$$t_{\text{hold}} < t_{\text{ccq}} + t_{\text{cd}}$$
$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

# Timing Analysis

 

$$t_{pd} =$$

$$t_{cd} =$$

Setup time constraint:

$$T_c \geq$$

$$f_c = 1/T_c =$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$


$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

# Timing Analysis

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \left[ \begin{array}{l} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{array} \right.$$

Hold time constraint:


$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ? \text{ No!}$$



# Fixing Hold Time Violation

## Add buffers to the short paths:

 

$$t_{pd} =$$

$$t_{cd} =$$

## Setup time constraint:

$$T_c \geq$$

$$f_c =$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$


per gate  $\left[ \begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$

## Hold time constraint:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

# Fixing Hold Time Violation

Add buffers to the short paths:

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$\text{per gate} \begin{cases} t_{pd} = 35 \text{ ps} \\ t_{cd} = 25 \text{ ps} \end{cases}$$


Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$

 
# Clock Skew

- The clock doesn't arrive at all registers at the same time
- Skew is the difference between two clock edges
- Examine the worst case to guarantee that the dynamic discipline is not violated for any register – many registers in a system!



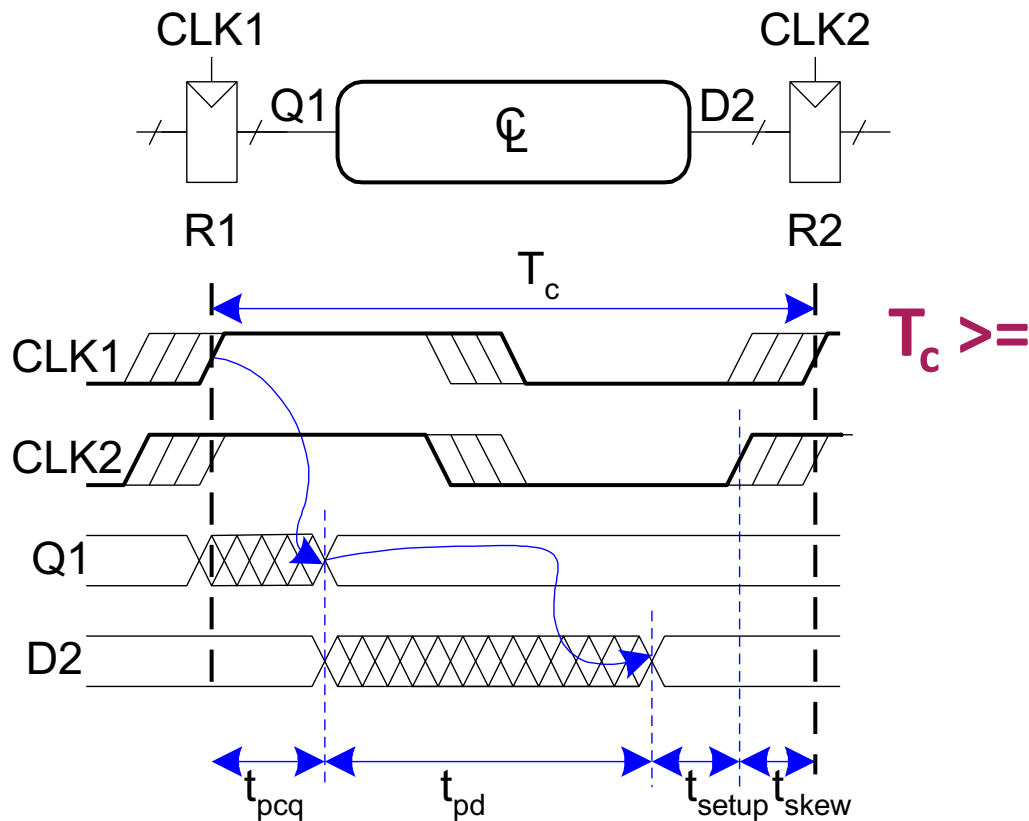
# Setup Time Constraint with Clock Skew

- In the worst case, the CLK2 is **earlier** than CLK1


 
# Setup Time Constraint with Clock Skew

- In the worst case, the CLK2 is **earlier** than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

$$t_{pd} \leq$$
 
# Setup Time Constraint with Clock Skew

- In the worst case, the CLK2 is **earlier** than CLK1




$$T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$$

$$t_{pd} \leq T_c - (t_{pcq} + t_{setup} + t_{skew})$$
 
# Hold Time Constraint with Clock Skew


- In the worst case, CLK2 is **later** than CLK1



$$t_{hold} + t_{skew} \leq$$
 
# Hold Time Constraint with Clock Skew

- In the worst case, CLK2 is **later** than CLK1




$$t_{hold} + t_{skew} \leq t_{ccq} + t_{cd}$$

$$t_{cd} \geq$$


 
# Hold Time Constraint with Clock Skew

- In the worst case, CLK2 is **later** than CLK1





$$t_{hold} + t_{skew} \leq t_{ccq} + t_{cd}$$

$$t_{cd} \geq t_{hold} + t_{skew} - t_{ccq}$$

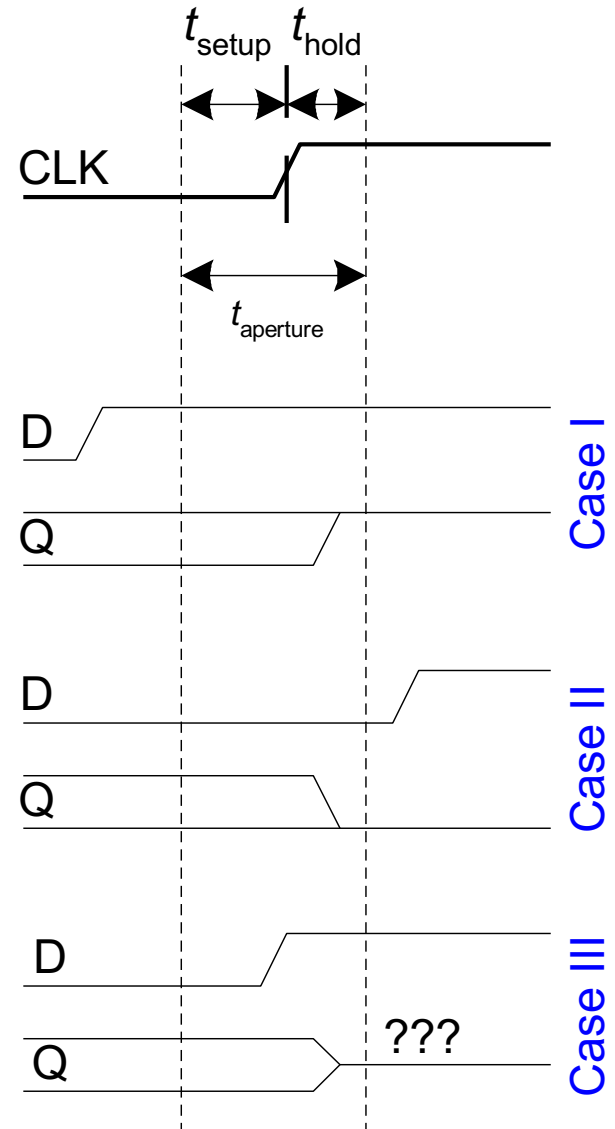 
# Violating the Dynamic Discipline

- Asynchronous (for example, user) inputs might violate the dynamic discipline


 
# Metastability

- Any bi-stable device has two stable states and a metastable state between them
- A flip-flop has two stable states (1 and 0) and one metastable state
- If a flip-flop lands in the metastable state, it could stay there for an undetermined amount of time



# Metastability


- $T_0/T_c$  describes the probability that the input changes at a bad time, i.e., during the aperture time

$$P(t_{\text{res}} > t) = (T_0/T_c) e^{-t/\tau}$$

- $\tau$  is a time constant indicating how fast the flip-flop moves away from the metastable state; it is related to the delay through the cross-coupled gates in the flip-flop
- In short, if a flip-flop samples a metastable input, if you wait long enough ( $t$ ), the output will have resolved to 1 or 0 with high probability.

 
# Synchronizers

- Asynchronous inputs (D) are inevitable (user interfaces, systems with different clocks interacting, etc.).
- The goal of a synchronizer is to make the probability of failure (the output Q still being metastable) low.
- A synchronizer cannot make the probability of failure 0.


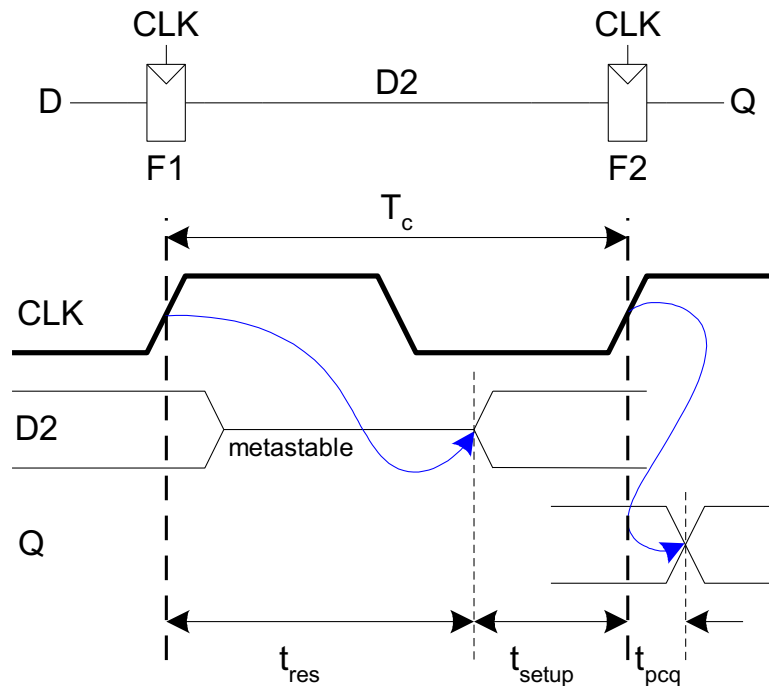
# Synchronizer Internals


- A synchronizer can be built with two back-to-back flip-flops.
- Suppose the input D is changing when it is sampled by F1.
- Internal signal D2 has  $(T_c - t_{\text{setup}})$  time to resolve a 1 or 0.


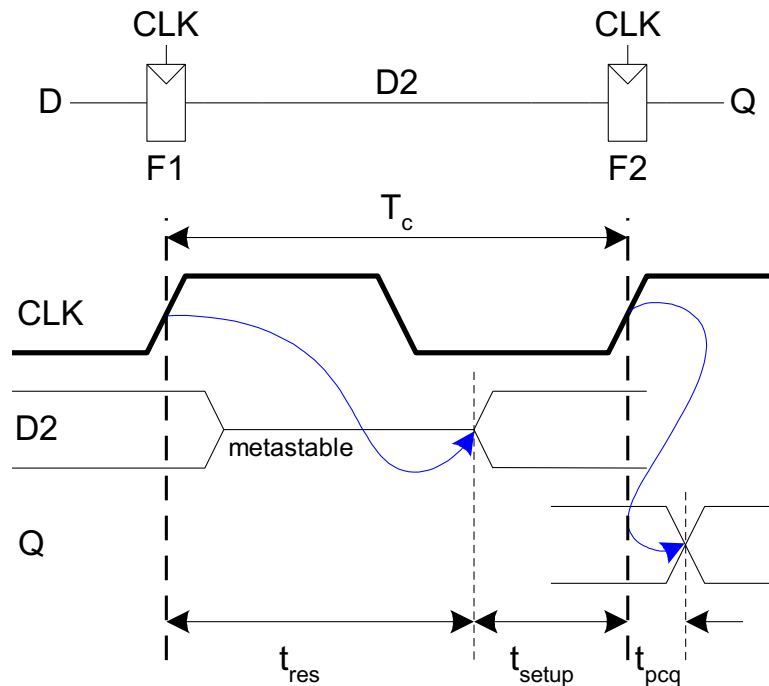
# Synchronizer Probability of Failure

- For each sample, the probability of failure of this synchronizer is:

$$P(\text{failure}) = \frac{T_0}{T_c} e^{-\frac{T_c - t_{\text{setup}}}{\tau}}$$



# Synchronizer Mean Time Before Failure

- If the asynchronous input changes once per second, the probability of failure per second of the synchronizer is simply  $P(\text{failure})$ .
- In general, if the input changes  $N$  times per second, the probability of failure per second of the synchronizer is:


$$P(\text{failure})/\text{sec} = N \frac{T_0}{T_c} e^{-\frac{T_c - t_{\text{setup}}}{\tau}}$$

- Thus, the synchronizer fails, on average,  $1/[P(\text{failure})/\text{second}]$   
This is called the mean time between failures, MTBF:

$$MTBF = \frac{1}{P(\text{failure})/\text{sec}} = \frac{T_c e^{\frac{T_c - t_{\text{setup}}}{\tau}}}{NT_0}$$



# Example Synchronizer

 

Suppose:  $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$

$T_0 = 150 \text{ ps}$

$N = 10 \text{ events per second}$

$\tau = 200 \text{ ps}$

$t_{\text{setup}} = 100 \text{ ps}$

What is the probability of failure? MTBF?

$P(\text{failure}) =$


$=$

$P(\text{failure})/\text{second} =$

$=$

MTBF  $=$

# Example Synchronizer

 

Suppose:  $T_c = 1/500 \text{ MHz} = 2 \text{ ns}$        $\tau = 200 \text{ ps}$   
 $T_0 = 150 \text{ ps}$        $t_{\text{setup}} = 100 \text{ ps}$   
 $N = 10 \text{ events per second}$

What is the probability of failure? MTBF?

$$P(\text{failure}) = (150 \text{ ps} / 2 \text{ ns}) e^{-(1.9 \text{ ns}) / 200 \text{ ps}}$$

$$= 5.6 \times 10^{-6}$$

$$P(\text{failure})/\text{second} = 10 \times (5.6 \times 10^{-6})$$

$$= 5.6 \times 10^{-5} / \text{second}$$

$$\text{MTBF} = 1/[P(\text{failure})/\text{second}] \approx 5 \text{ hours}$$

# What did we learn ?

- **Timing constraints for sequential circuits**
  - *Setup time*, time needed for the inputs to be present before clock
  - *Hold time*, time needed after the clock where inputs should not change
  - *Aperture time*, time around clock event where inputs should stay stable
- **Problems related to clock skew**
- **Metastability and Synchronization**