

Memories

Digital Design and Computer Architecture

Mohammad Sadrosadati

Frank K. Gürkaynak

<http://safari.ethz.ch/ddca>


What will we learn today?

- **One more common sequential building block**
 - Counters
- **How can we store data?**
- **Array organization of memories**


Counters

- **Increments on each clock edge.**
 - Used to cycle through numbers. For example,
 - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- **Example uses:**
 - Digital clock displays
 - Program counter: keeps track of current instruction executing

Symbol

 

Implementation

 

Motivation: Memory Elements

■ Memories are large blocks

- A significant portion of a modern circuit is memory.


■ Memories are practical tools for system design

- Programmability, reconfigurability all require memory


■ Allows you to store data and work on stored data

- Not all algorithms are designed to process data as it comes, some require data to be stored.
- Data type determines required storage
 - SMS: 160 bytes
 - 1 second normal audio: 64 kbytes
 - 1 HD picture: 7.32 Mbytes

 Die photograph of an Intel processor in 45nm



Larger Memory Blocks

 

How can we store data

- **Flip-Flops (or Latches)**
 - Very fast, parallel access
 - Expensive (one bit costs 20+ transistors)

How can we store data

- **Flip-Flops (or Latches)**

- Very fast, parallel access
- Expensive (one bit costs 20+ transistors)

- **Static RAM (we will describe them in a moment)**

- Relatively fast, only one data word at a time
- Less expensive (one bit costs 6 transistors)

How can we store data

■ Flip-Flops (or Latches)

- Very fast, parallel access
- Expensive (one bit costs 20+ transistors)

■ Static RAM (we will describe them in a moment)

- Relatively fast, only one data word at a time
- Less expensive (one bit costs 6 transistors)

■ Dynamic RAM (we will describe them a bit later)

- Slower, reading destroys content (refresh), one data word at a time, needs special process
- Cheaper (one bit is only a transistor)

How can we store data

■ Flip-Flops (or Latches)

- Very fast, parallel access
- Expensive (one bit costs 20+ transistors)

■ Static RAM (we will describe them in a moment)

- Relatively fast, only one data word at a time
- Less expensive (one bit costs 6 transistors)

■ Dynamic RAM (we will describe them a bit later)

- Slower, reading destroys content (refresh), one data word at a time, needs special process
- Cheaper (one bit is only a transistor)

■ Other storage technology (hard disk, flash)

- Much slower, access takes a long time, non-volatile
- Per bit cost is lower (no transistors directly involved)


Array Organization of Memories

- **Efficiently store large amounts of data**

- Consists of a memory array (stores data)
- Address selection logic (selects one row of the array)
- Readout circuitry (reads data out)



- **An M-bit value can be read or written at each unique N-bit address**

 - All values can be accessed, but only M-bits at a time
- Access restriction allows more compact organization



Memory Arrays

  
- **Two-dimensional array of bit cells**
 - Each bit cell stores one bit
- **An array with N address bits and M data bits:**
 - 2^N rows and M columns
 - Depth: number of rows (number of words)
 - Width: number of columns (size of word)
 - Array size: depth \times width = $2^N \times M$



| Address | Data | | | |
|---------|-----------|---|---|-----------------|
| 11 | 0 | 1 | 0 | ↑ depth ↓ |
| 10 | 1 | 0 | 0 | |
| 01 | 1 | 1 | 0 | |
| 00 | 0 | 1 | 1 | |
| | ↔ width ↔ | | | |


Memory Array: Example

 - $2^2 \times 3$ -bit array
- Number of words: 4
- Word size: 3-bits
- For example, the 3-bit word stored at address 10 is 100



| Address | Data | | | |
|---------|----------------------|---|---|------------------------------|
| 11 | 0 | 1 | 0 | <div>↑ depth ↓</div> |
| 10 | 1 | 0 | 0 | |
| 01 | 1 | 1 | 0 | |
| 00 | 0 | 1 | 1 | |
| | <div>← width →</div> | | | |

Memory Arrays

 


Types of Memories

- **Volatile memories (loses data when power is off)**
 - Static Random Access Memory (SRAM)
 - Dynamic Random Access Memory (DRAM)
- **Non-volatile memories (keeps data even without power)**
 - Read Only Memory (ROM)
 - Various forms of flash memory (i.e. EEPROM)

Static Random Access Memory


 
- **Volatile:** Stores data by cross coupled inverters, once data is stored the inverters keep the value (therefore static)



- Historically called Random Access Memory, because data can be accessed in any order (unlike magnetic tapes which allowed only serial access)

Dynamic Random Access Memory

  
- **Volatile:** Stores data by charging a (small) capacitor



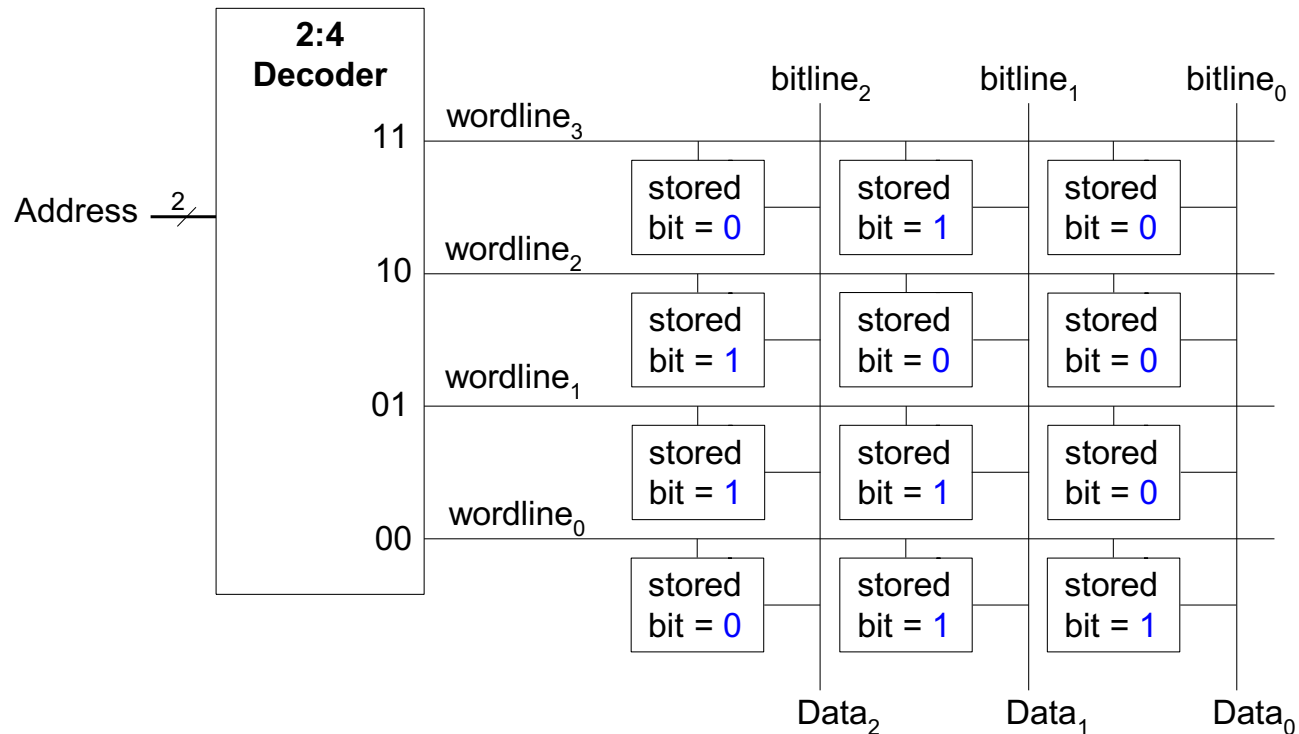- Problem is that the charge on the capacitor will slowly discharge (memory will forget the value) with time.
- It is called Dynamic, because we have to refresh the contents before memory forgets what it stored.
- The larger the capacitor, the longer it takes to forget
 - This costs area, ingenious methods are used to increase capacitance


Memory Array Organization

- Storage nodes in one column connected to one bitline
- Address decoder activates only ONE wordline
- Content of one line of storage available at output




Memory Array Organization

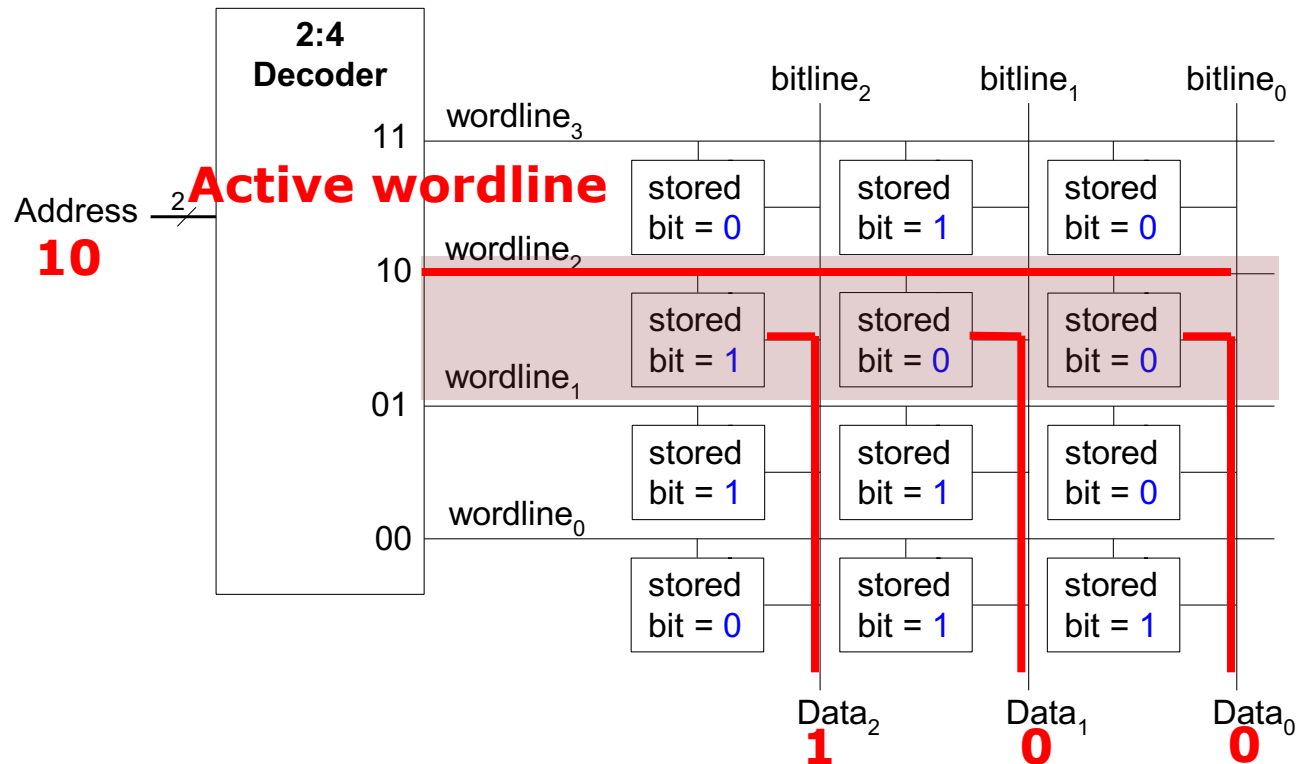- Storage nodes in one column connected to one bitline
- Address decoder activates only ONE wordline
- Content of one line of storage available at output



How is Access Controlled ?


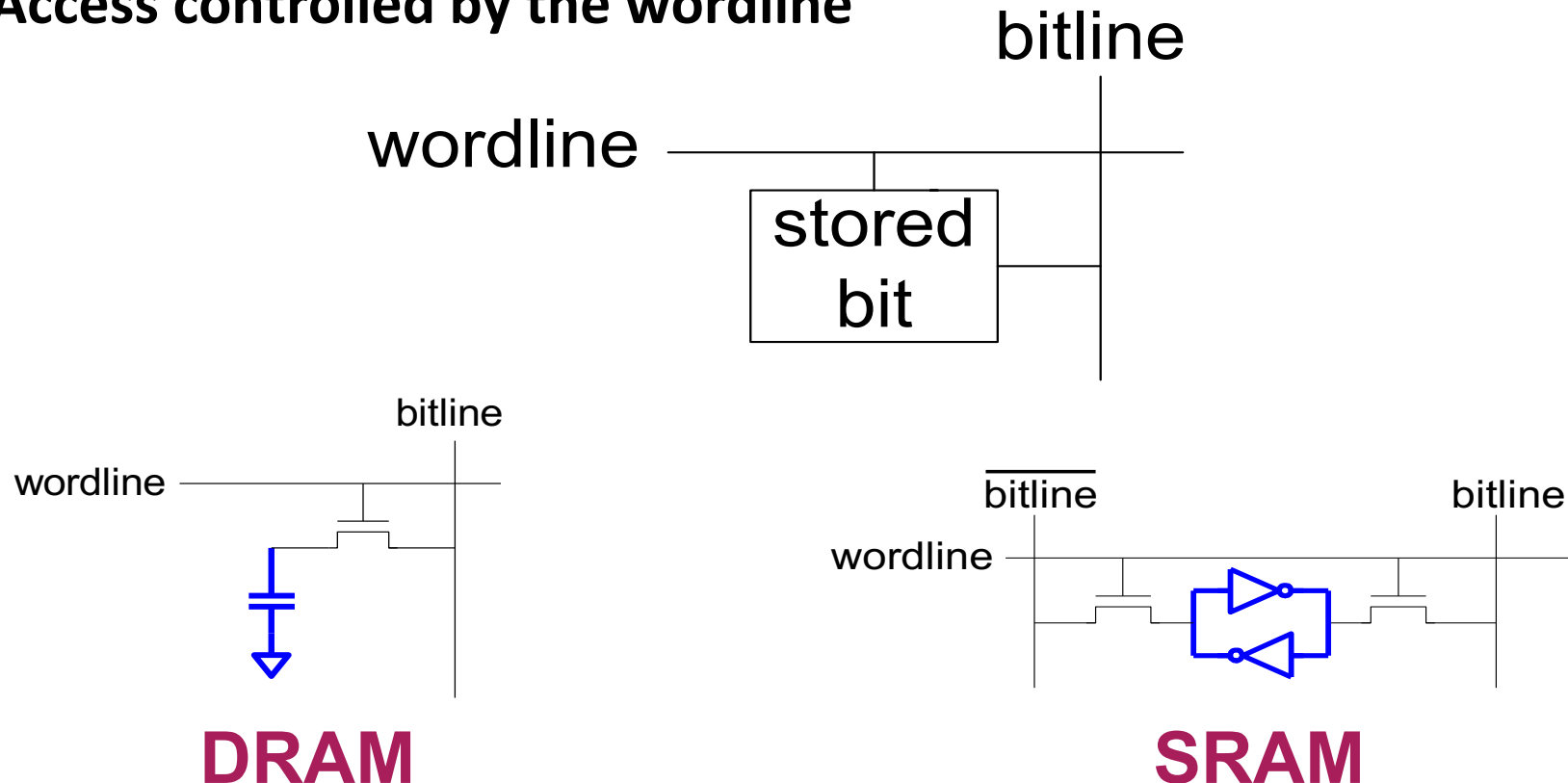
- Access transistors configured as switches connect the bit storage to the bitline.
- Access controlled by the wordline




Read Only Memories

- **Non Volatile: Read Only Memories (ROM) can be made much denser**
 - No need to change the content (no storage transistors)
 - Denser array
- **Used for keeping content that will not change**
 - Program of an embedded system
 - Configuration data
 - Look up tables
- **Re-writable (flash) memories are commonly used**
 - These are actually programmable, but writing is very slow
 - From an application point of view identical to ROMs

ROMs: Dot Notation

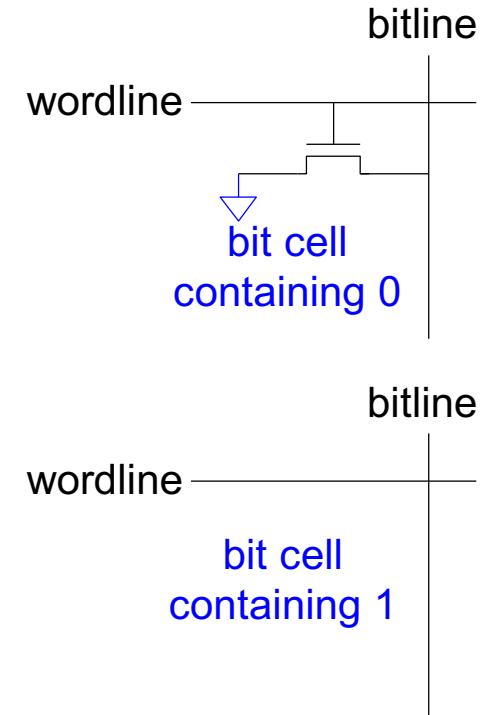 


ROM Storage

 

| Address | Data | | | depth ↑ ↓ |
|-------------|------|---|---|-----------------|
| 11 | 0 | 1 | 0 | |
| 10 | 1 | 0 | 0 | |
| 01 | 1 | 1 | 0 | |
| 00 | 0 | 1 | 1 | |
| width ←→ | | | | |

ROM Logic

 

$$Data_2 = A_1 \oplus A_0$$


$$Data_1 = \overline{A_1} + A_0$$

$$Data_0 = \overline{A_1} \overline{A_0}$$

Logic with Memory Arrays

- Implement the following logic functions using a 22×3 -bit memory array:

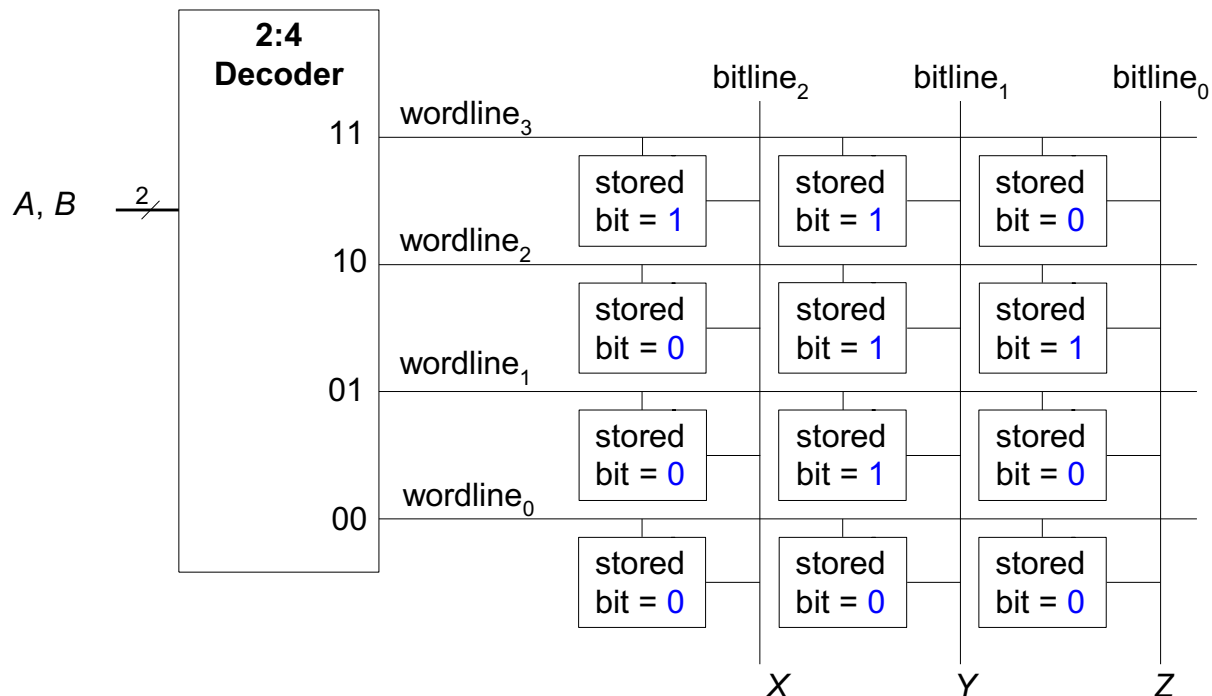
- $X = AB$
- $Y = A + B$
- $Z = A \overline{B}$



Logic with Memory Arrays


- Called lookup tables (LUTs): look up output at each input combination (address)

| Truth Table | | |
|-------------|---|---|
| A | B | Y |
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

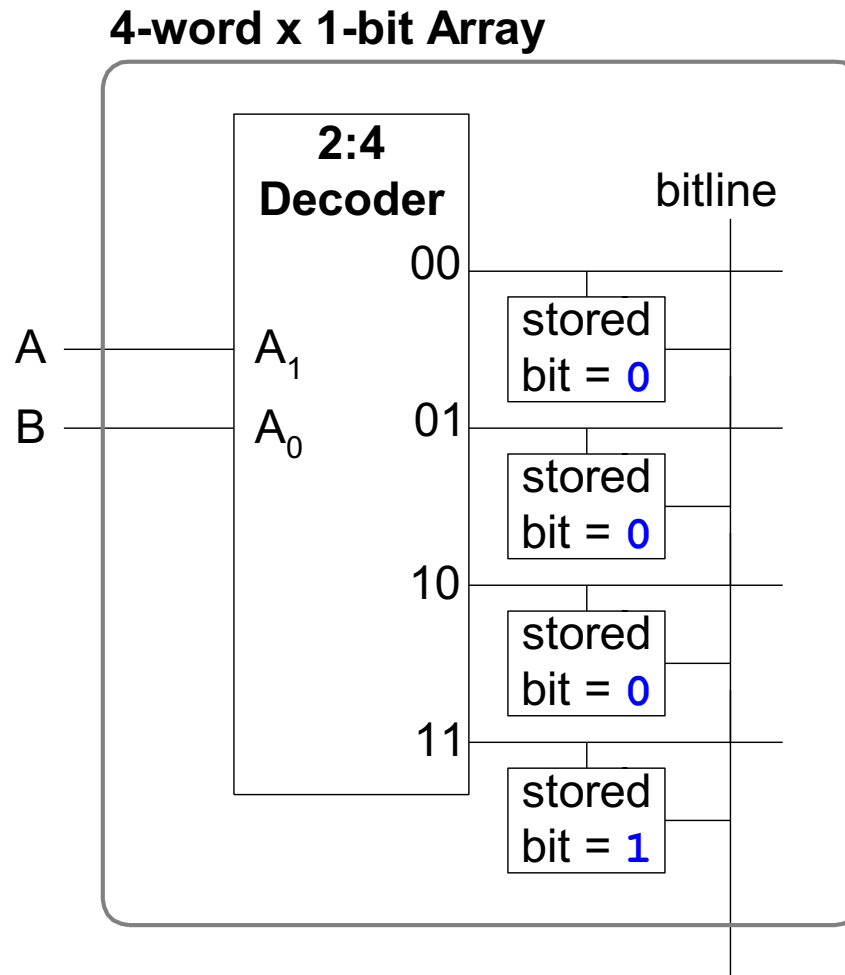

Multi-ported Memories

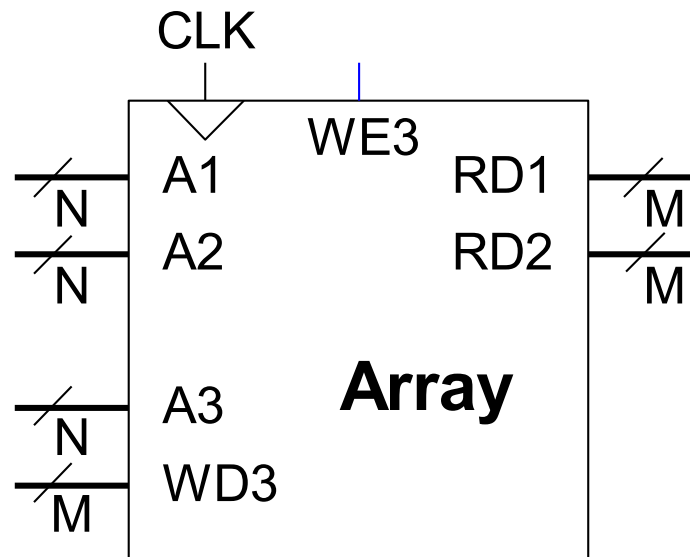- Port: address/data pair
- 3-ported memory:
 - 2 read ports (A_1/RD_1 , A_2/RD_2)
 - 1 write port (A_3/WD_3 , WE_3 enables writing)
- Small multi-ported memories are called register files



Memory Arrays in Verilog

```
// 256 x 3 memory module with one read/write port
module dmem( input      clk, // clock
             input      we,  // write enable
             input  [7:0] a   // 8-bit address
             input  [2:0] wd, // 3-bit write data
             output [2:0] rd); // 3-bit read data

    reg [2:0] RAM[255:0]; // Memory array, holds
                        // 256 entries each 3 bits wide

    assign rd = RAM[a]; // Read access

    always @(posedge clk) // with rising clock
        if (we)           // if write enable
            RAM[a] <= wd; // write data is stored in array
endmodule
```


What have we learned?

■ Different ways of storing data

- Registers
- Static Memory
- Dynamic Memory

■ Array organization

- Compact form
- One row active at a time